

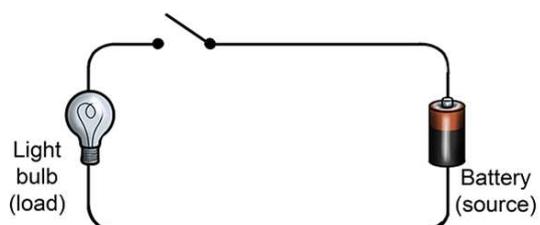


การควบคุมสวิตซ์ Switch Control

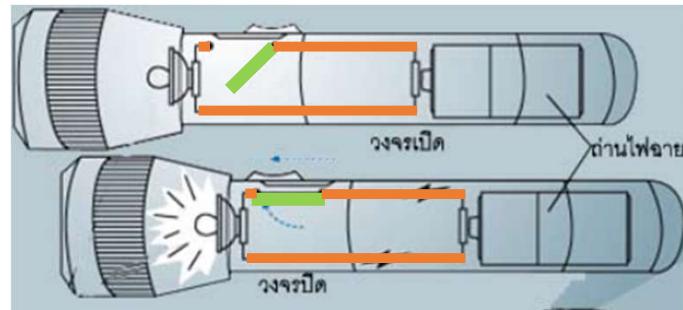


วงจรเปิด (Open Circuit)

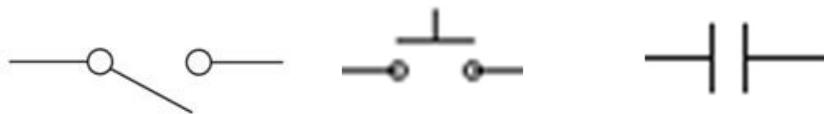- กระแสไฟฟ้าไม่สามารถไหลผ่านได้ ทำให้อุปกรณ์ไม่ทำงาน
- หน้าตัวสัมผัสไม่เชื่อมต่อกัน (Open Contact)



วงจรปิด (Close Circuit)

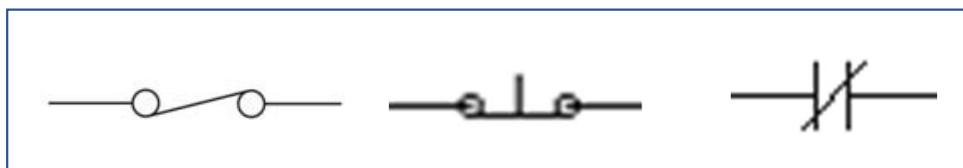- หน้าตัวสัมผัสเชื่อมต่อกัน (Close Contact)
- กระแสไฟฟ้าไหลในวงจรได้ ทำให้อุปกรณ์ทำงาน






Normally Open Contact



Normally Closed Contact



Changeover Contact

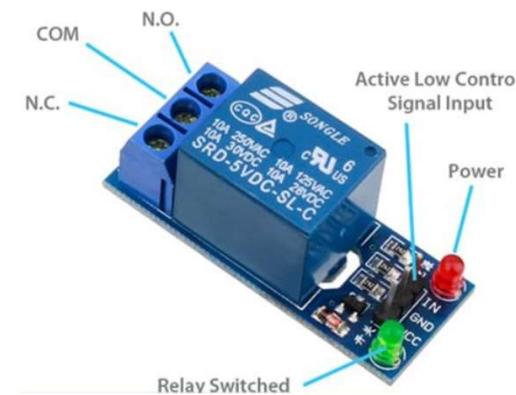





หมุนไปทาง MAN สั่งเปิดปิด
จากสวิตช์หน้าคู่





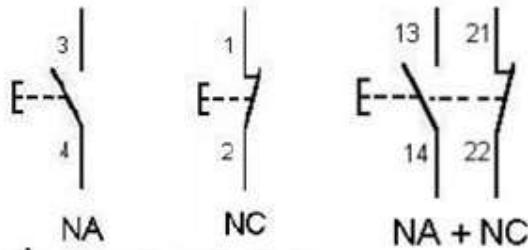
หมุนไปทาง AUTO รอเวลาที่ตั้งไว้
จาก timer



Light Switch Circuit

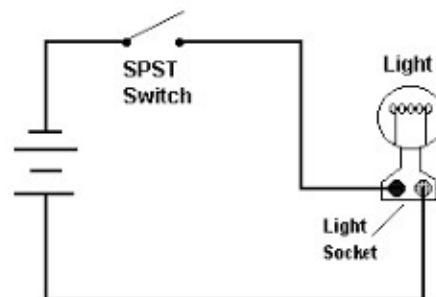


InstrumentationTools.com

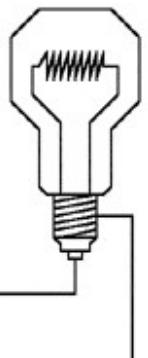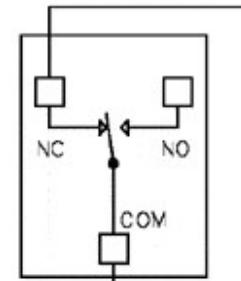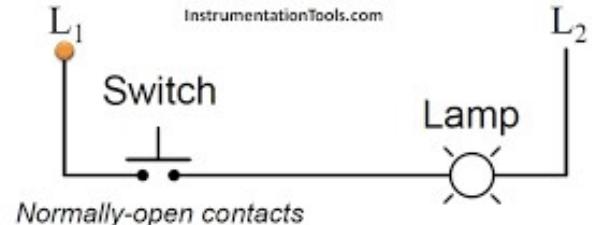

Light Relay Turns Off when
Turns On

วงจรเปิด (Open Circuit)

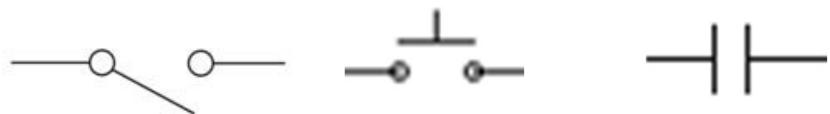
- กระแสไฟฟ้าไม่สามารถไหลผ่านได้ ทำให้อุปกรณ์ไม่ทำงาน
- หน้าสัมผัสไม่เชื่อมต่อกัน (**Open Contact**)



A Normal Open contact (NO)


วงจรปิด (Close Circuit)

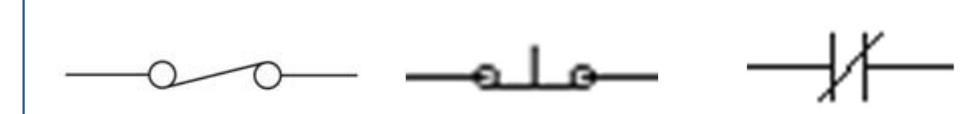- หน้าสัมผัสเชื่อมต่อกัน (**Close Contact**)
- กระแสไฟฟ้าไหลในวงจรได้ ทำให้อุปกรณ์ทำงาน







A Normal Closed contact (NC)




ปกติหน้าสัมผัสเปิด

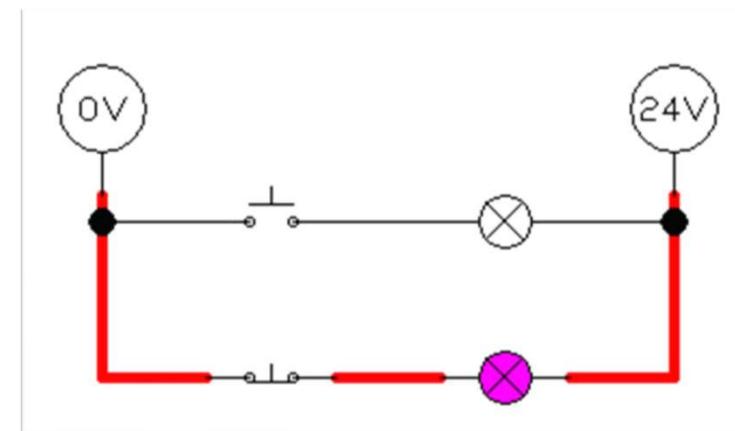





ปกติหน้าสัมผัสปิด

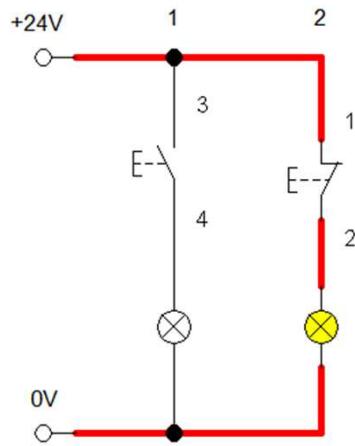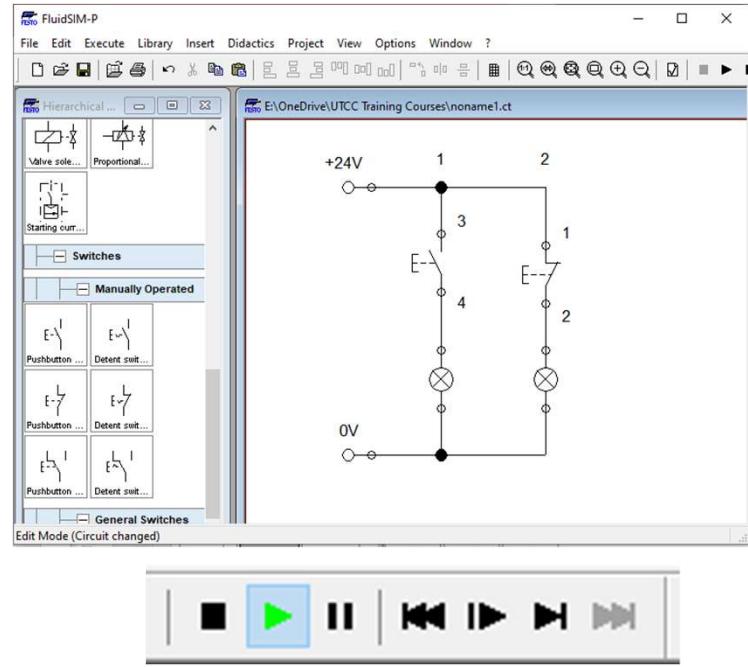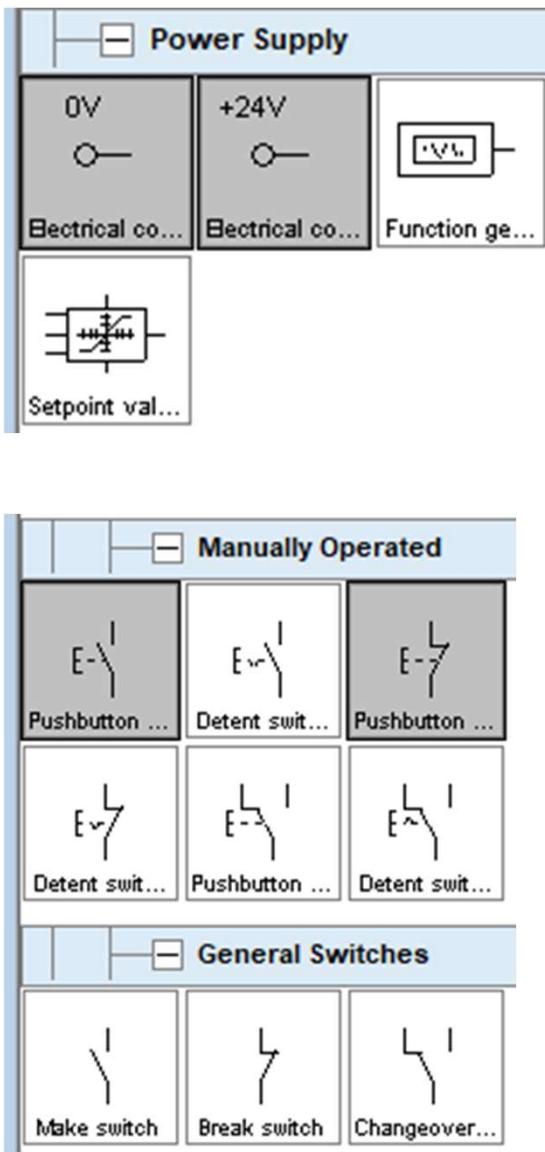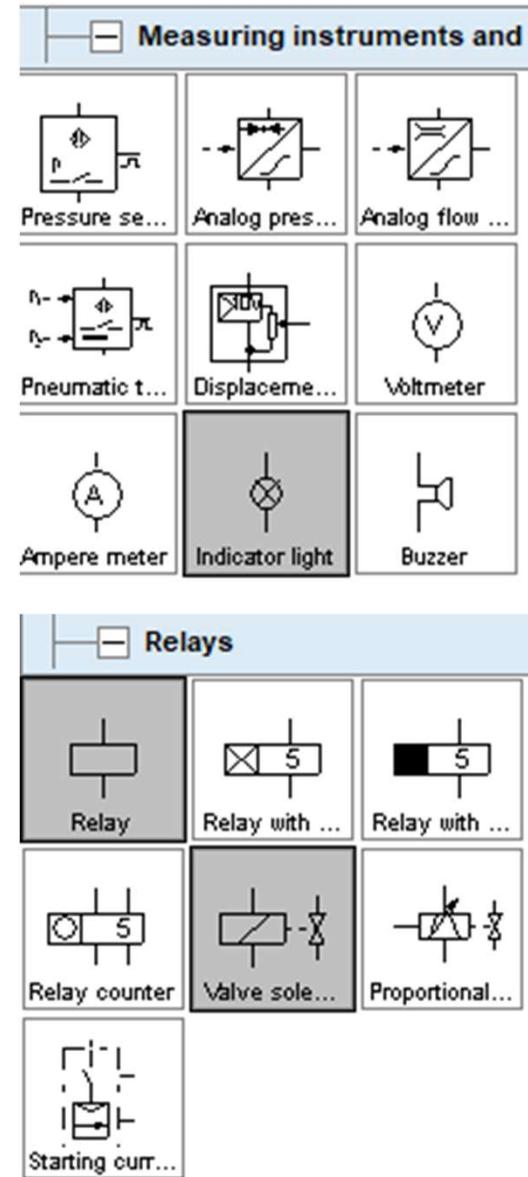


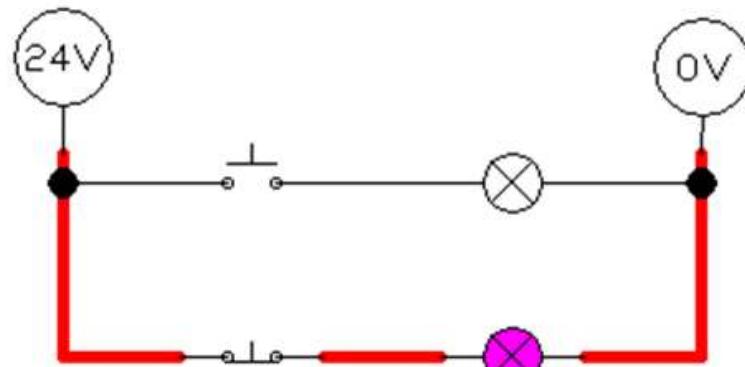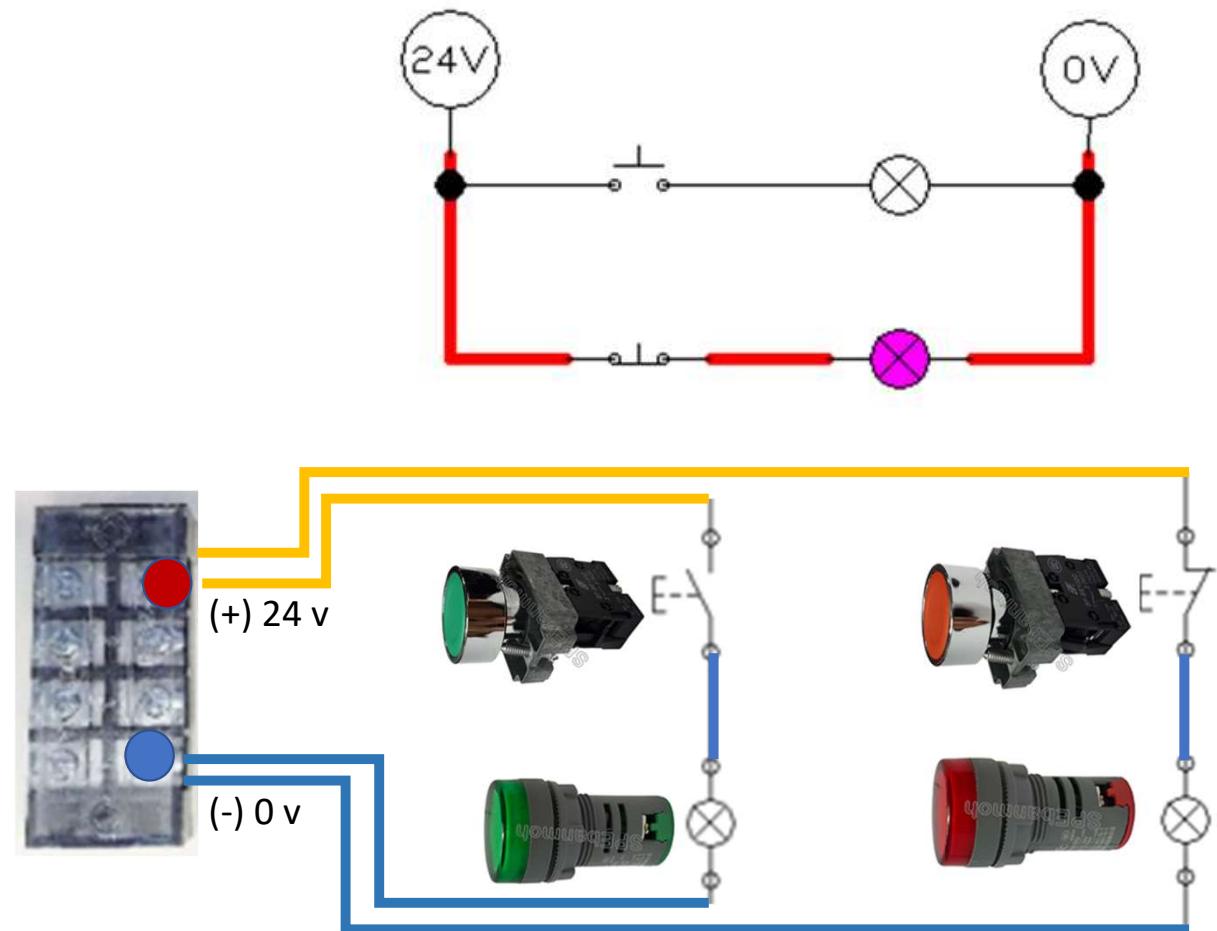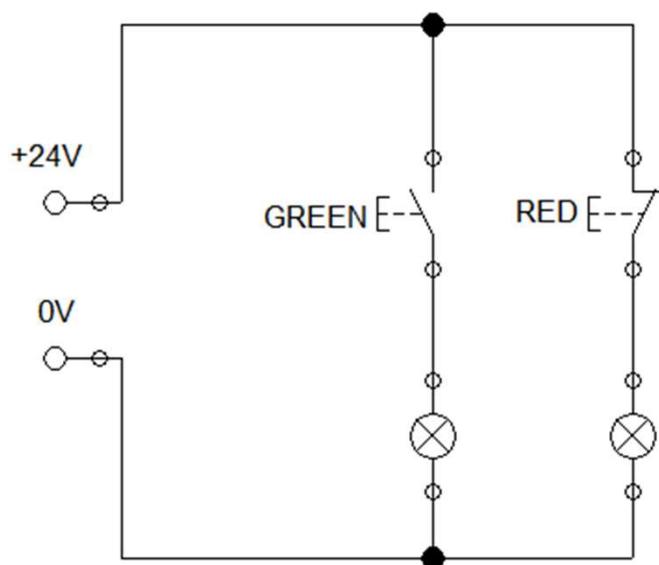Basic 01 - Switch Control (NO-NC) youtube




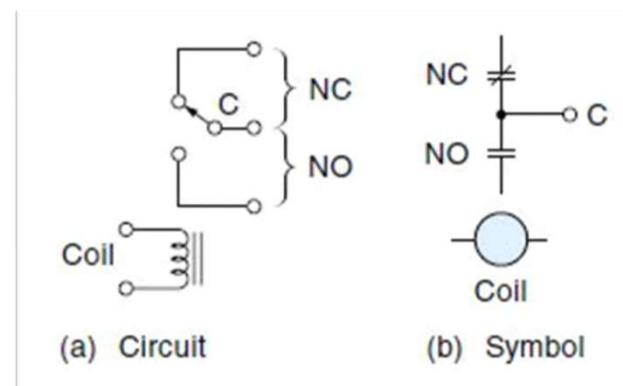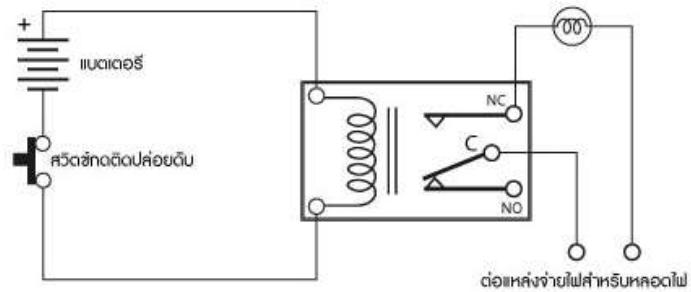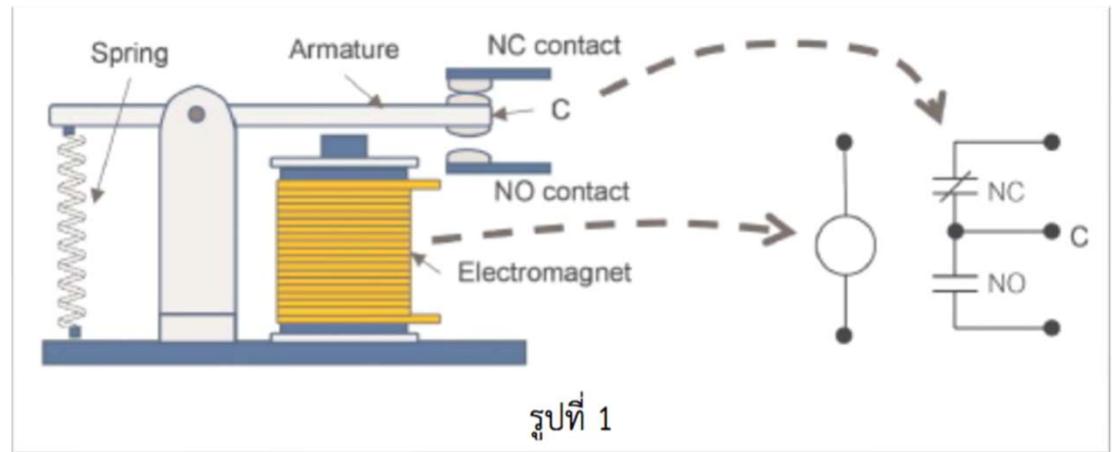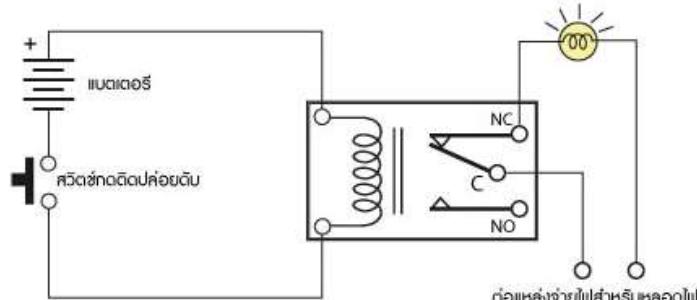รีเล耶 Relay (สวิตช์ ที่ใช้กระแสไฟฟ้าในสั่งงาน หน้าสัมผัสเปิดปิด)




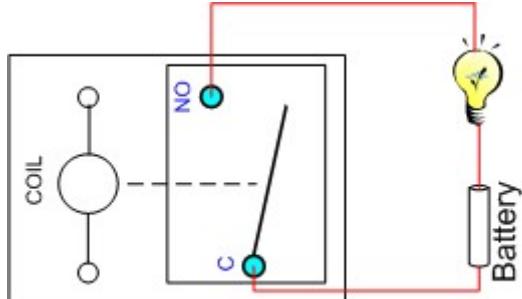


Single Pole, Single Throw (SPST)

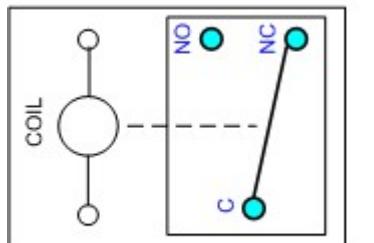


Single Pole, Double Throw (SPDT)

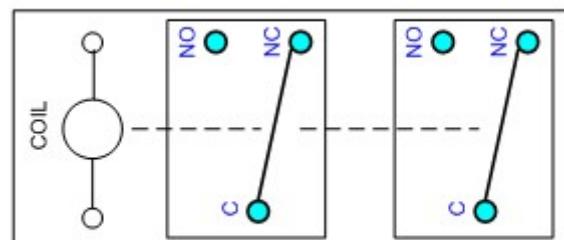

Double Pole, Double Throw (DPDT)

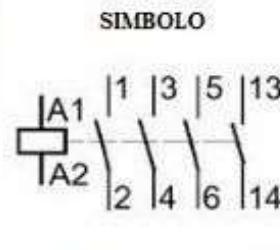


www.areatecnologia.com

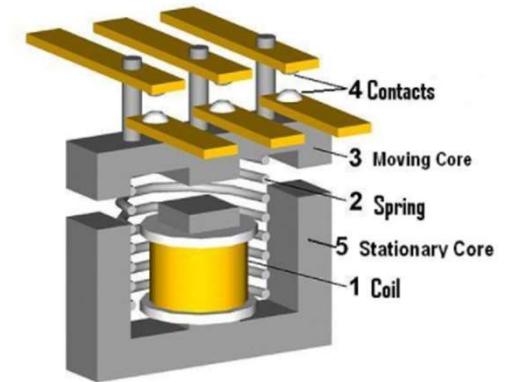





รีเลย์ Relay Switch





รูปที่ 2






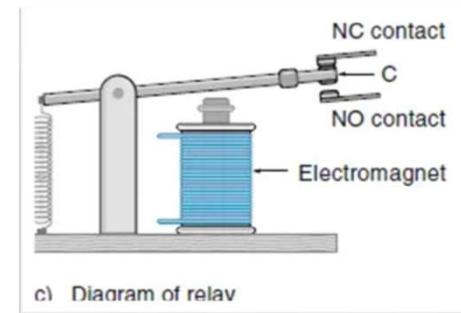


c) Diagram of relay

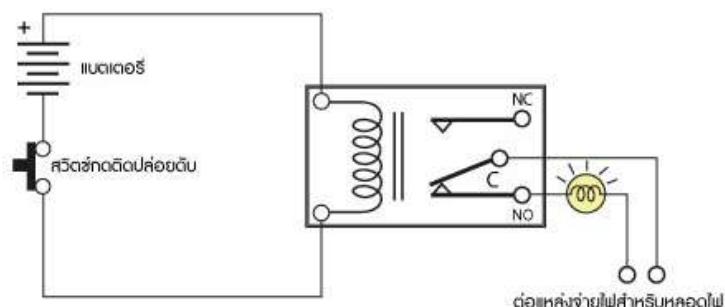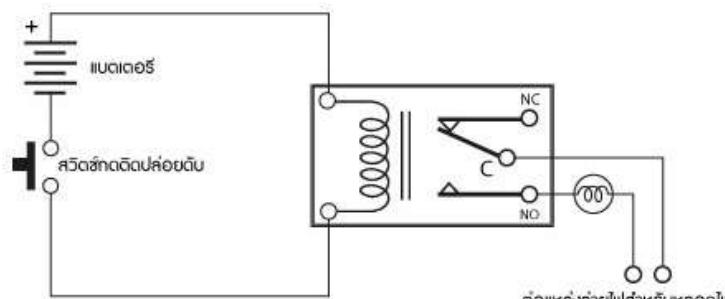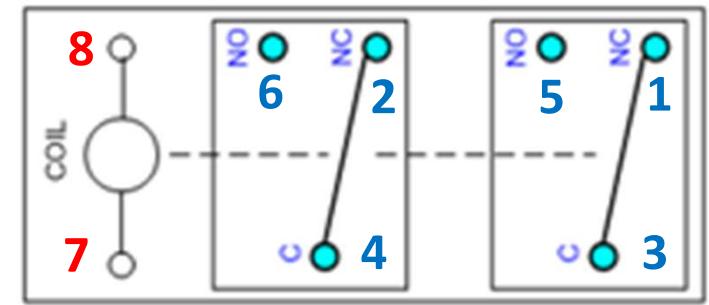
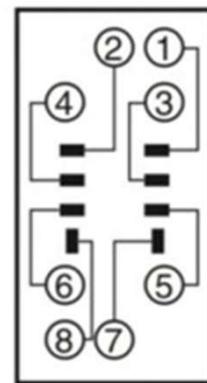


Normally Open Contact



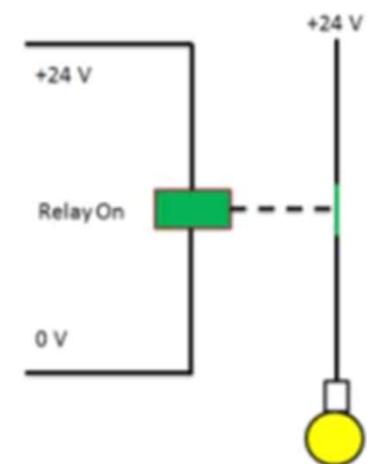
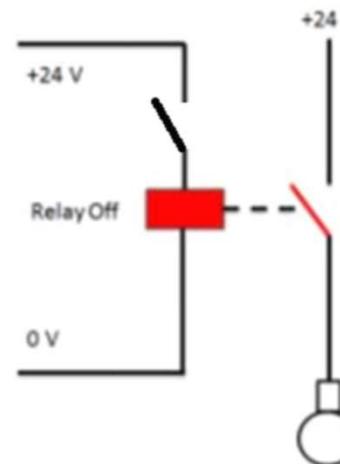


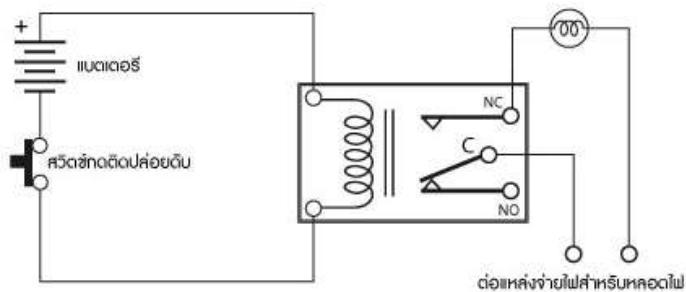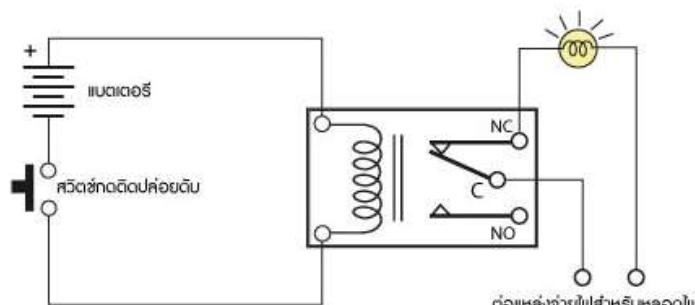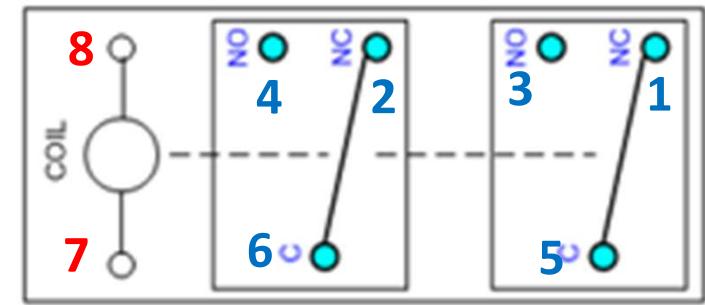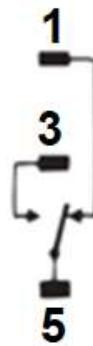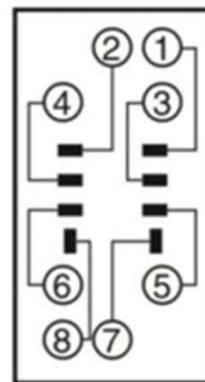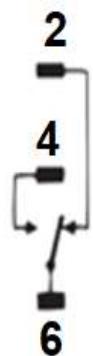






Normally Close Contact


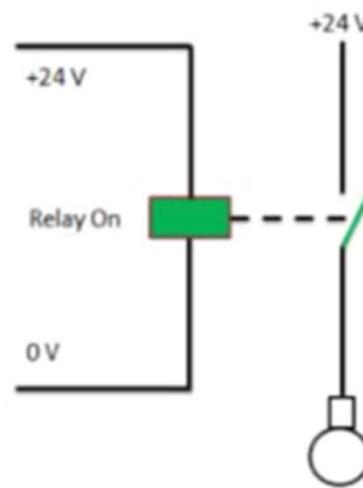
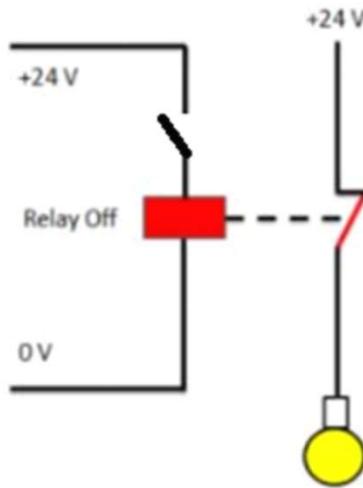


Basic 02 - Relay Control youtube

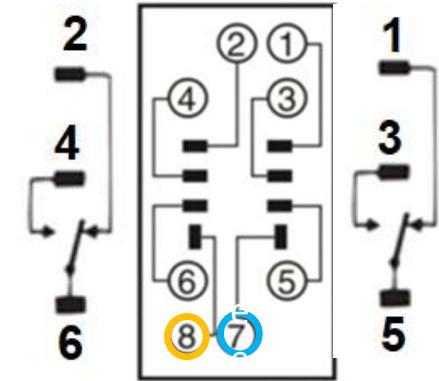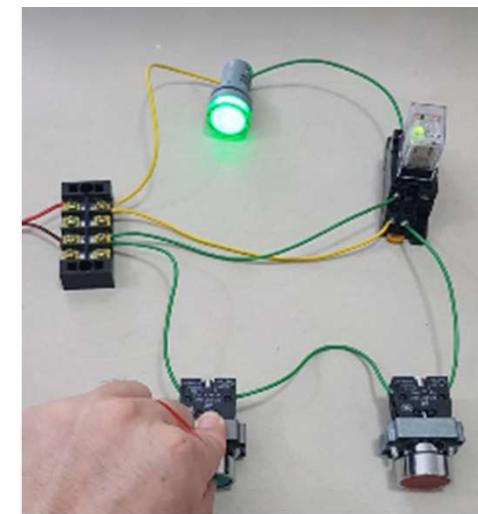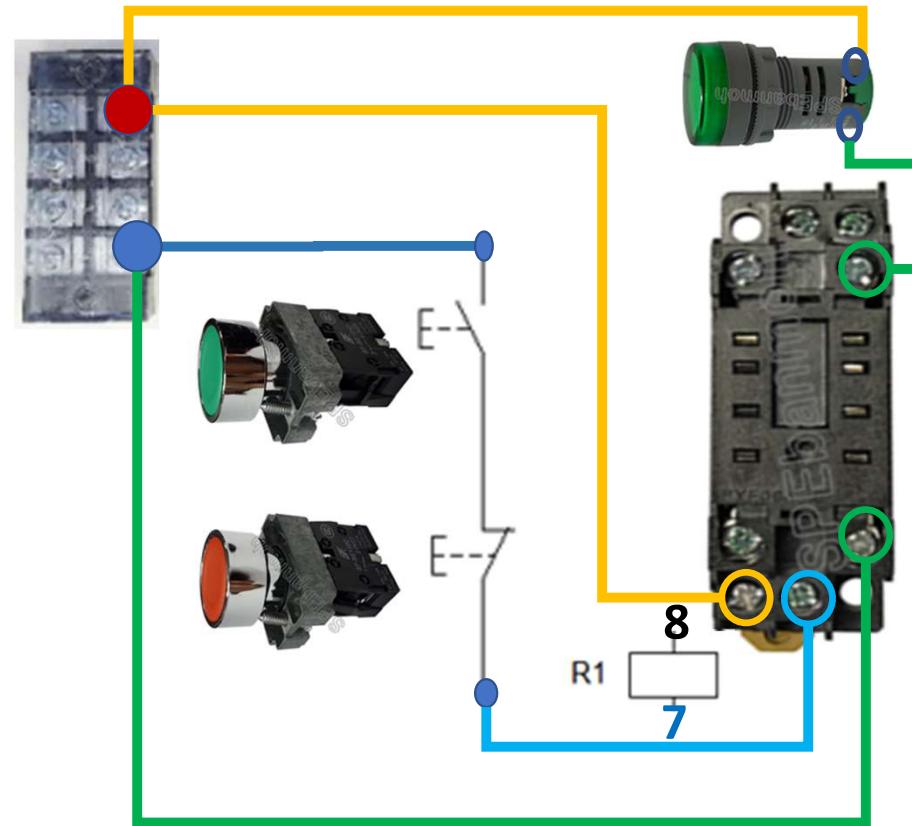
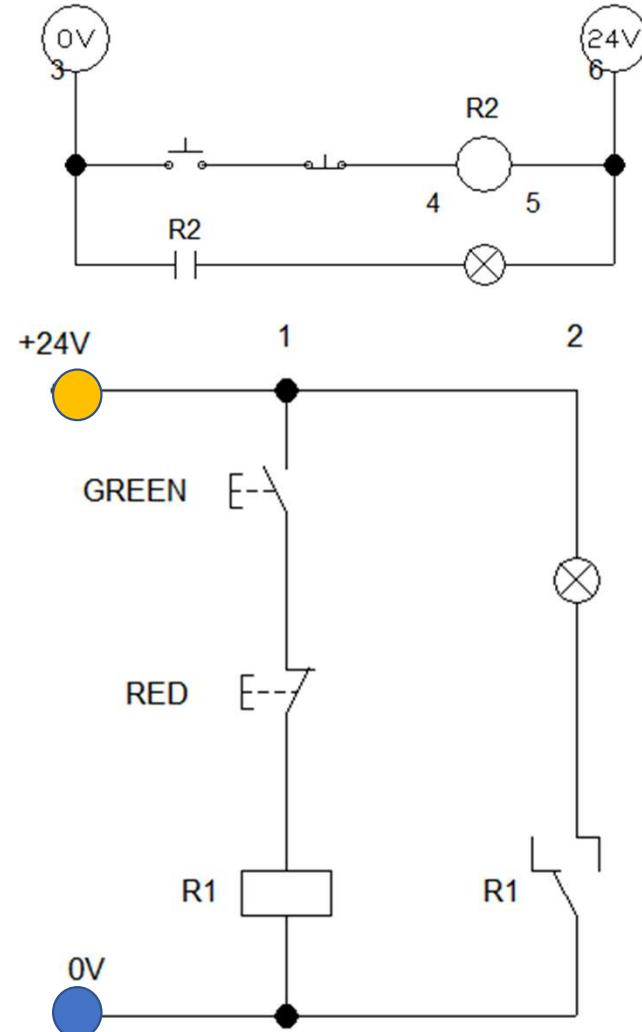


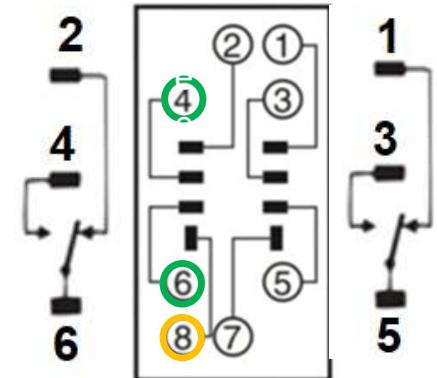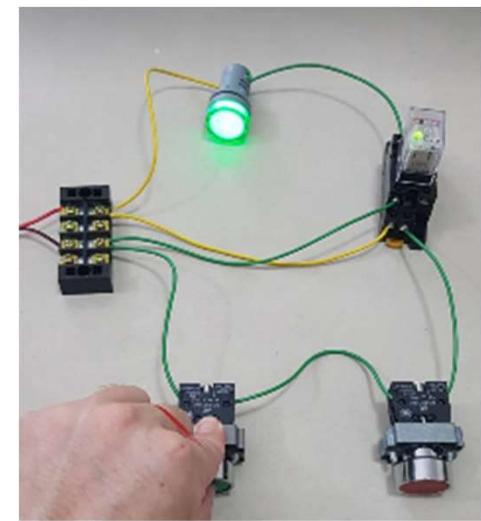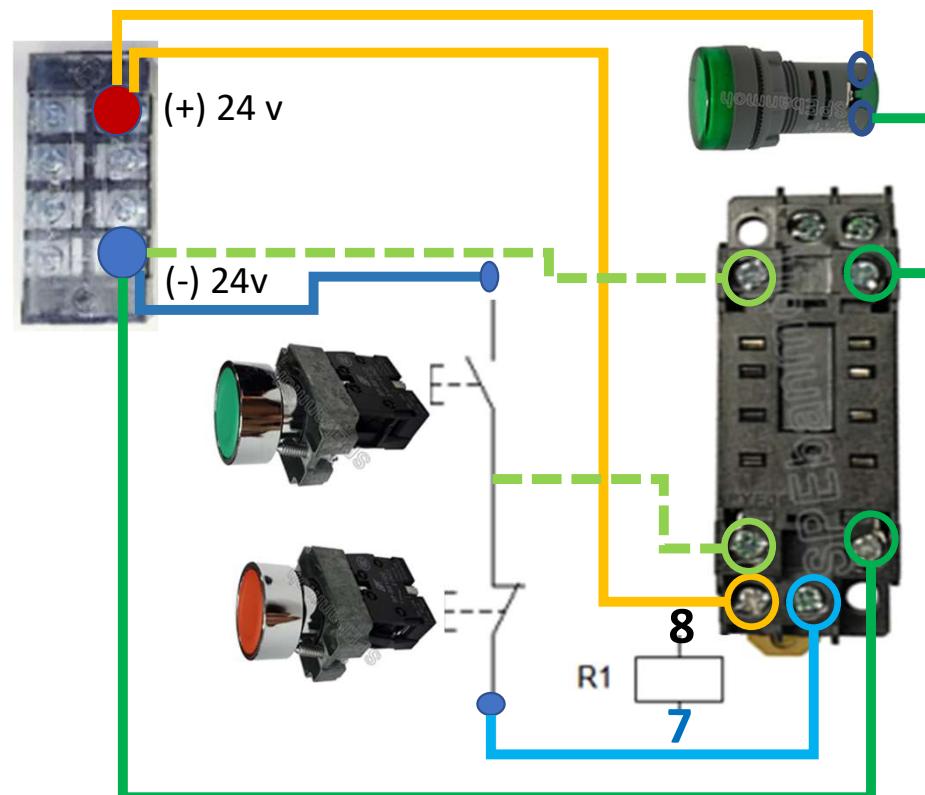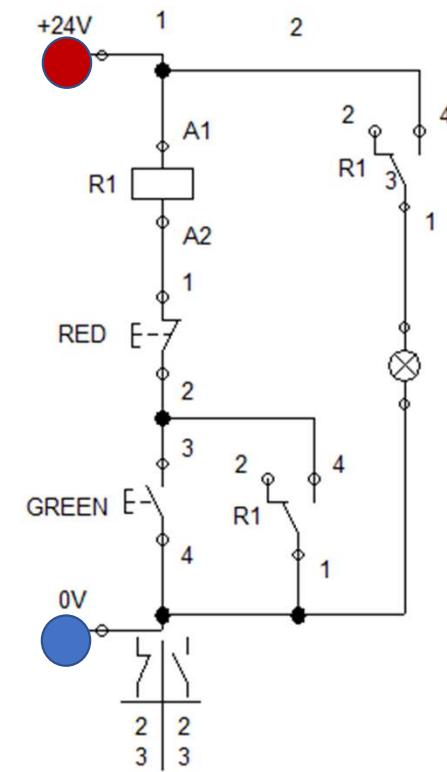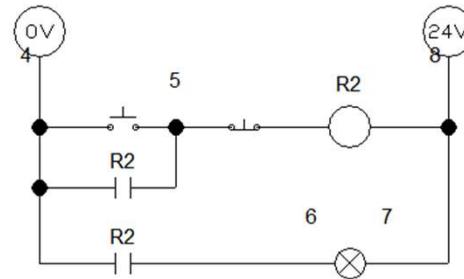Basic 03 - Relay Control (Self Holding) youtube




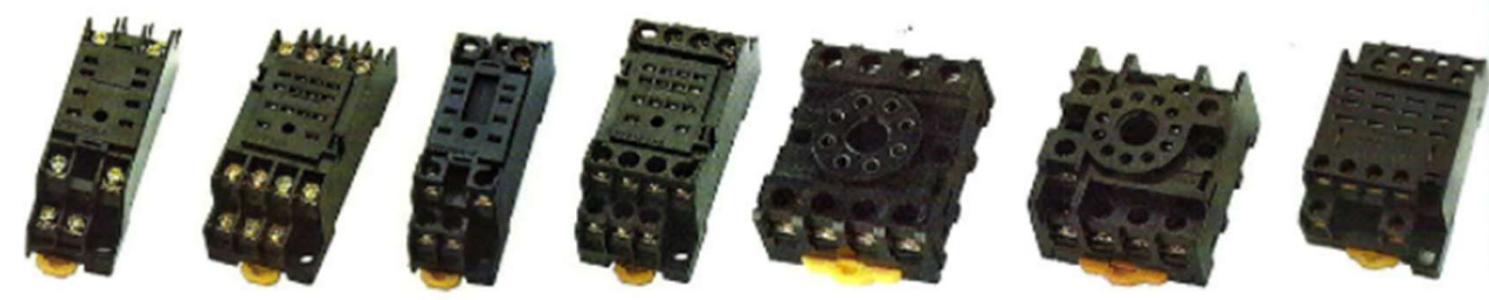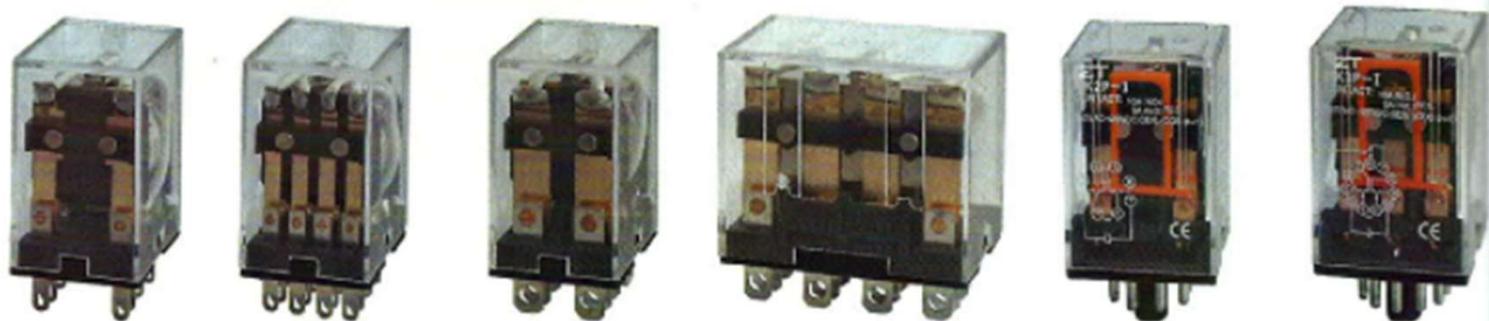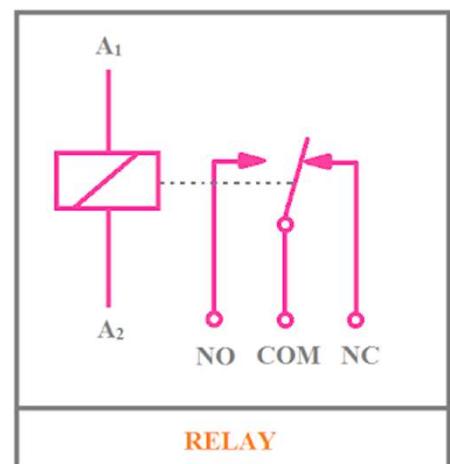


Specifications	Model	MY2 N	MY4 N	LY2	LY4	MK2P-I	MK3P-I
Contact capacity	AC Position	5A 250V	3A 250V	10A 250V	10A 250V	10A 250V	10A 250V
	DC	5A 30V	3A 30V	10A 30V	10A 30V	10A 30V	10A 30V

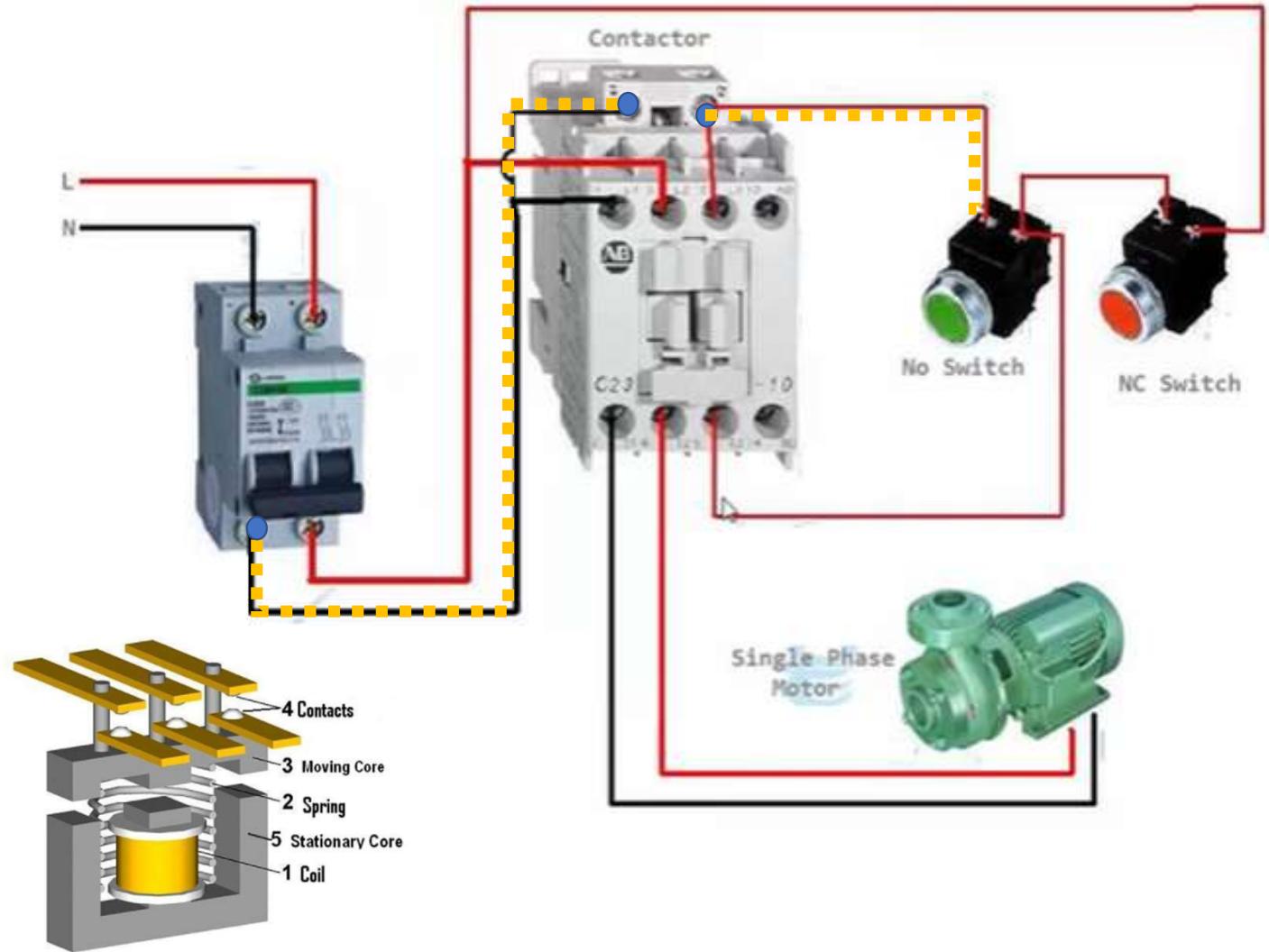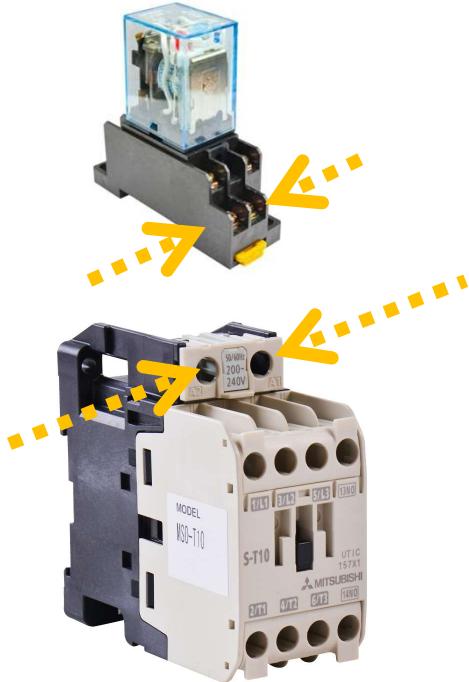




Timer

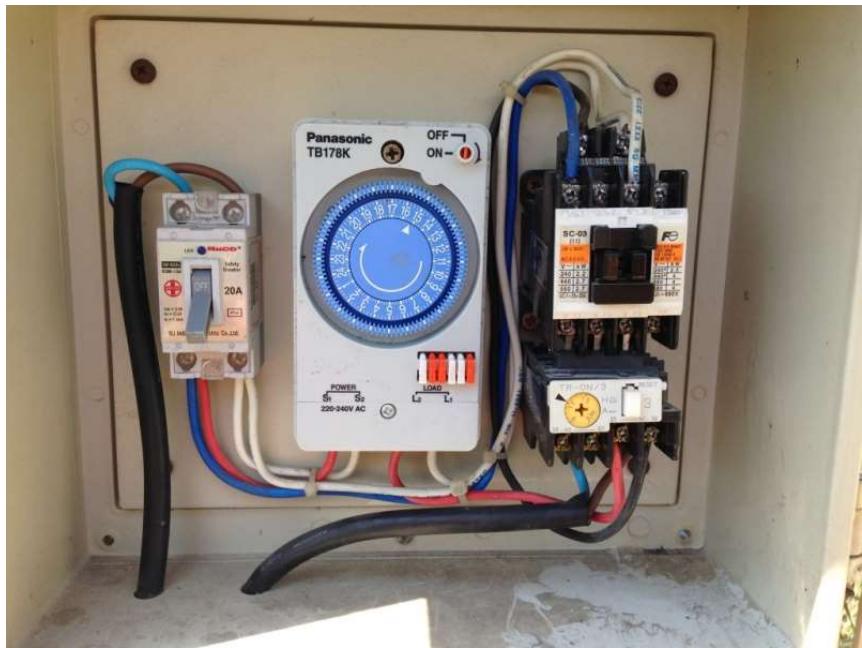


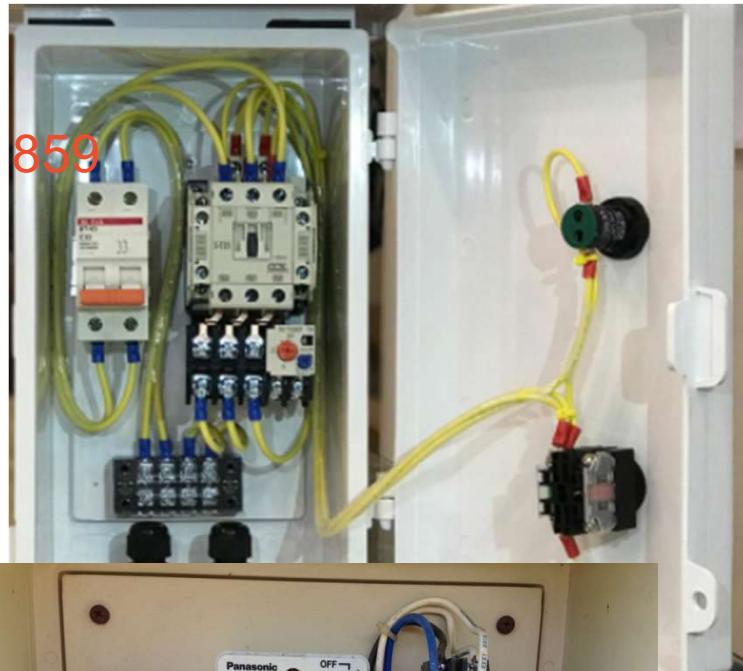



ตัวตั้งเวลา
Timer - 1,495

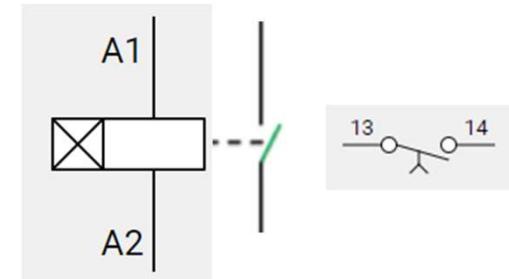

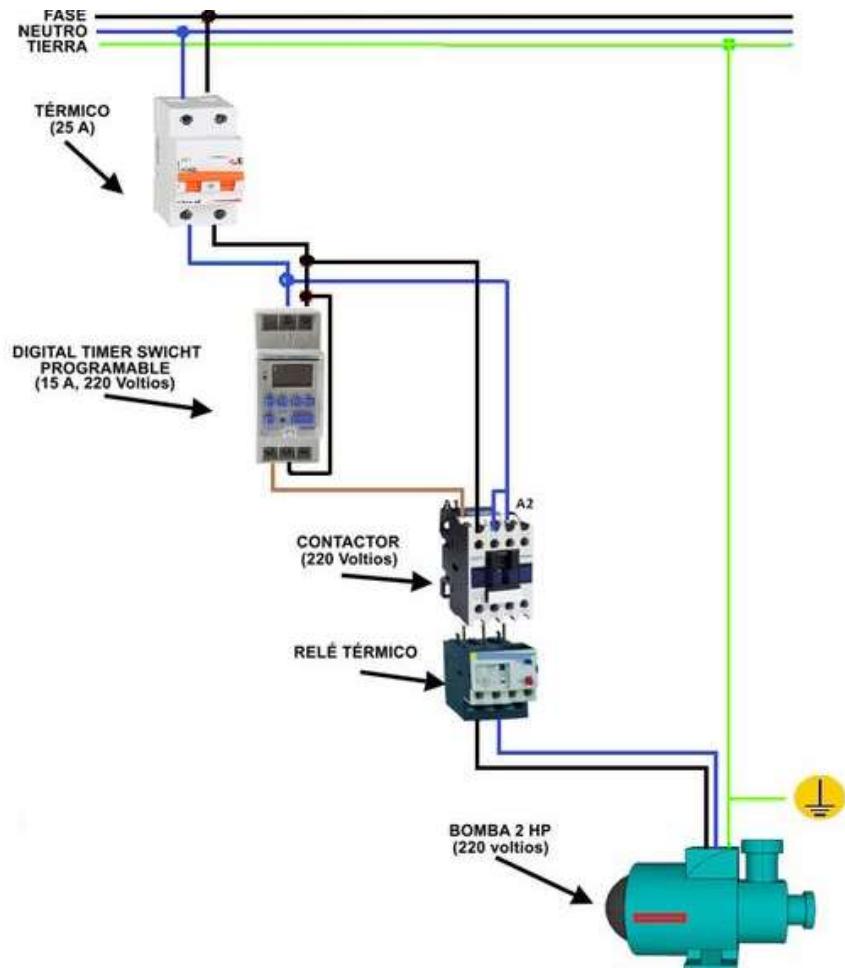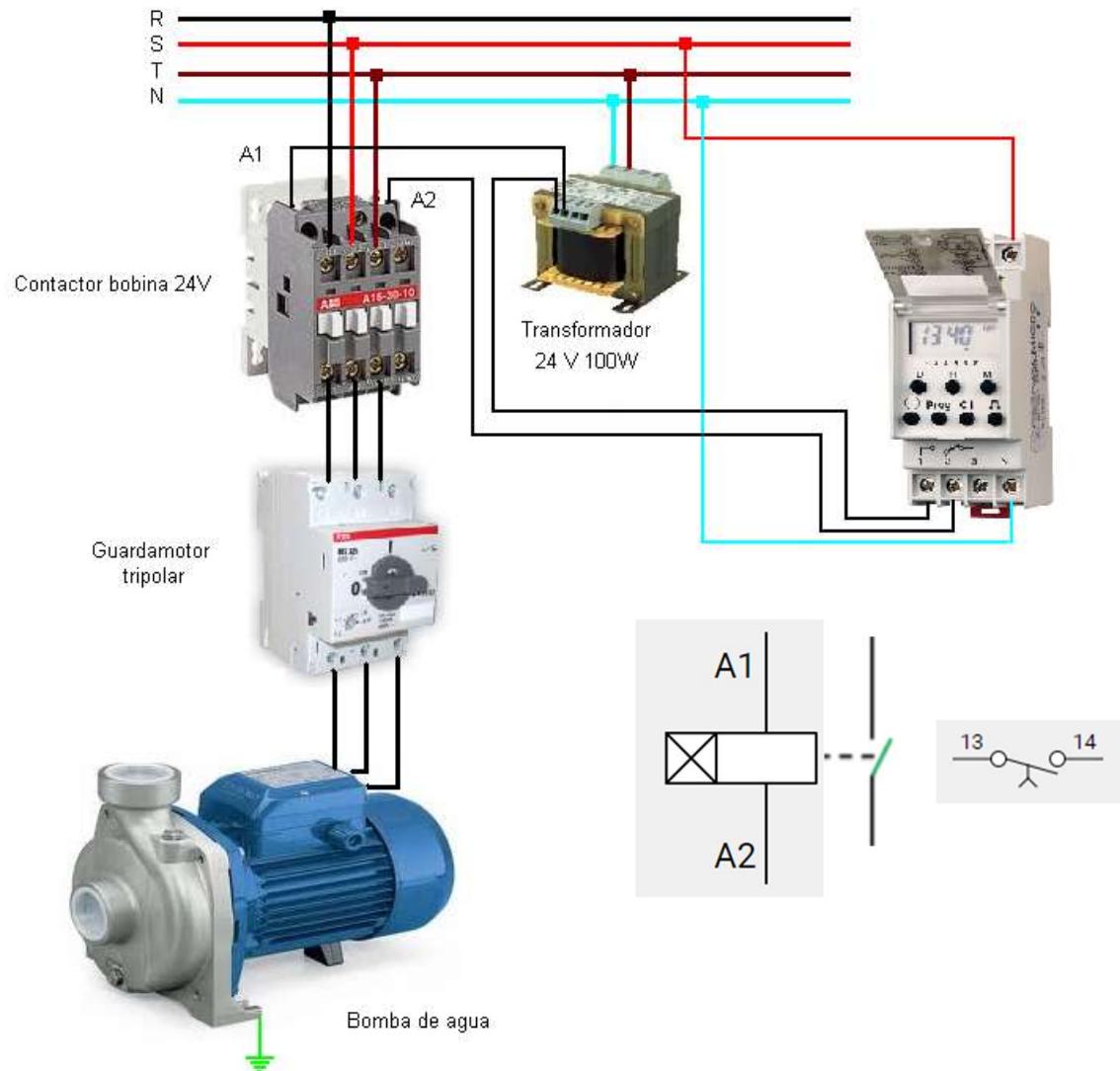

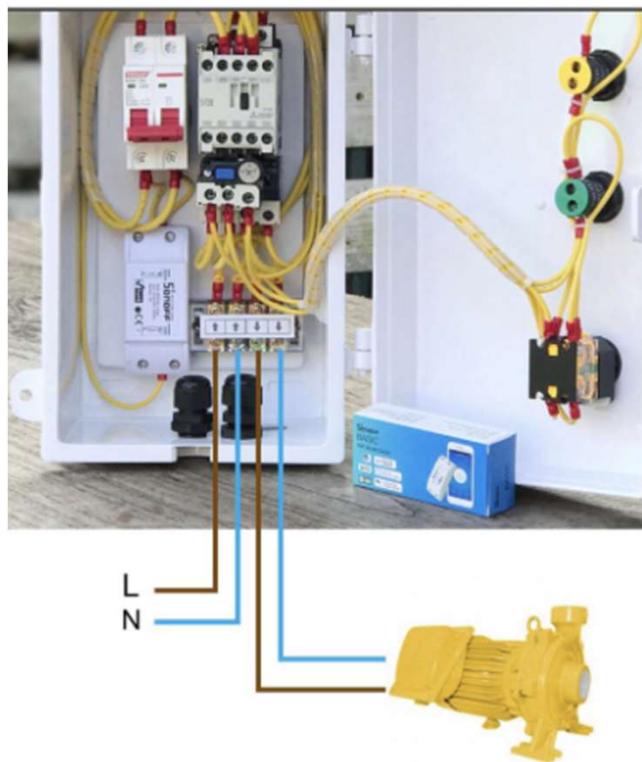


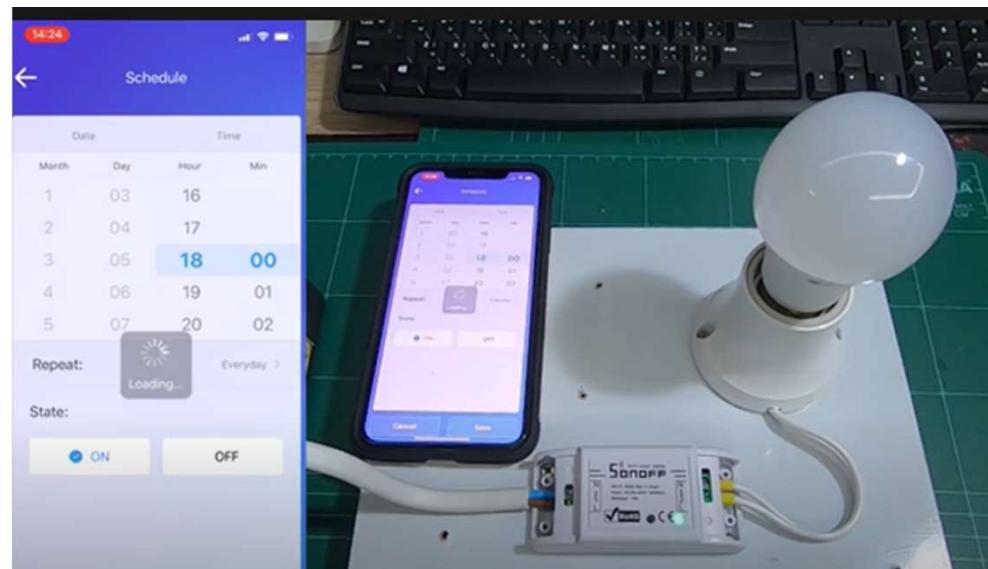





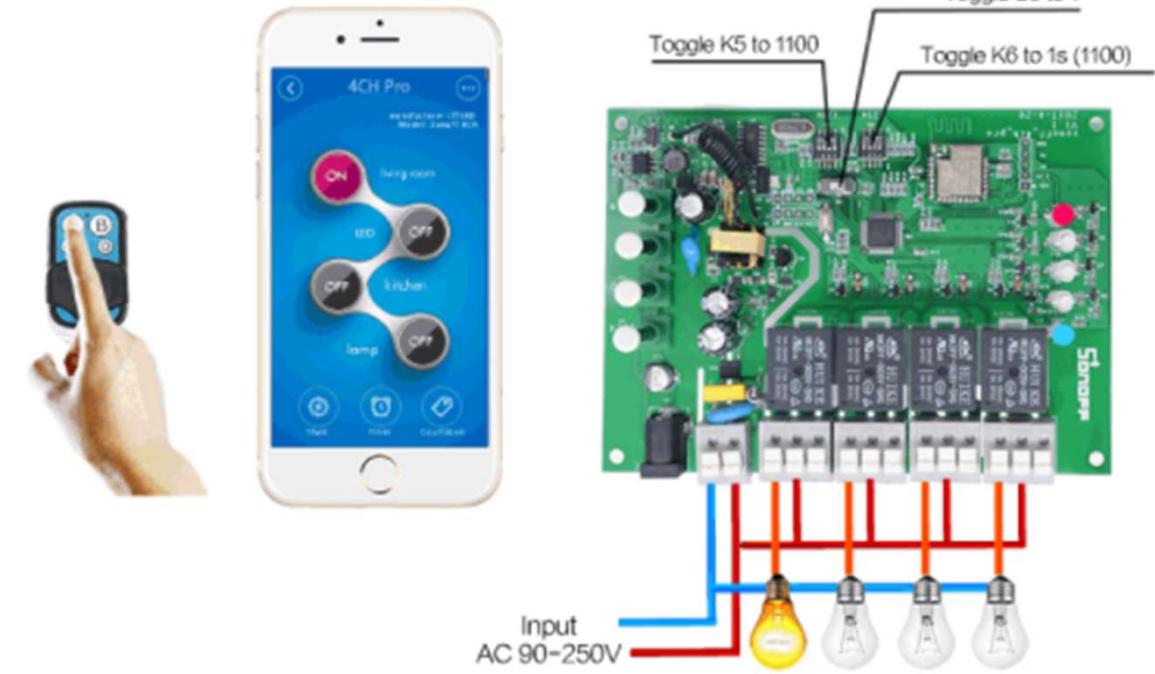



Sonoff 4CH Pro R3 ស៊ីថតសំងានផាន WiFi 4 ខែង
កេរមអីទូរទឹក RF



AC Motor Wiring Diagram


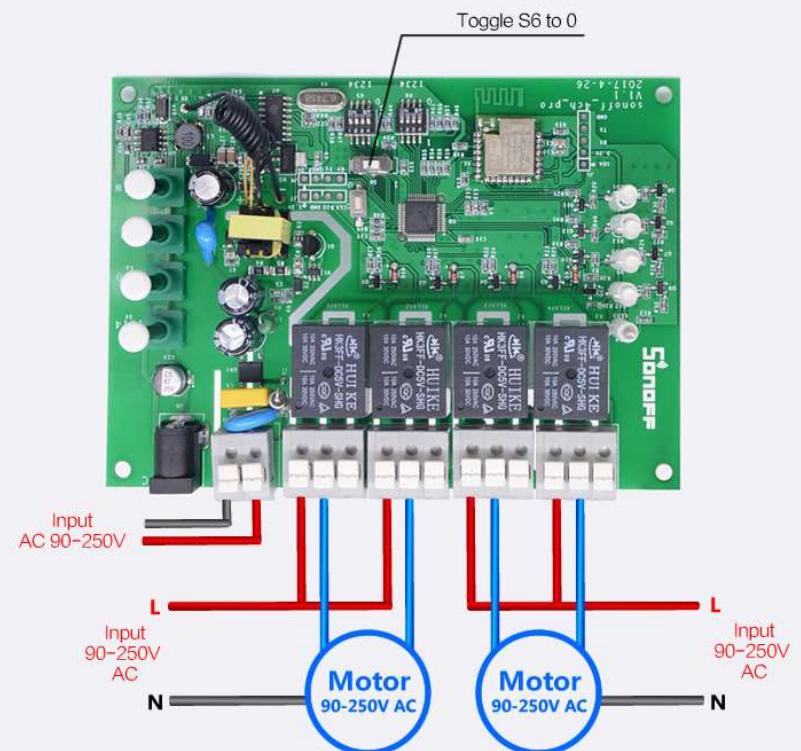



Note : only 1 motor can run each time.

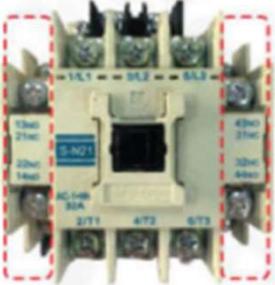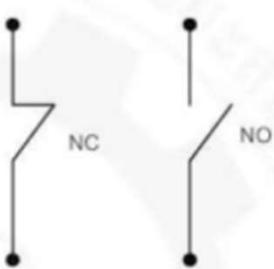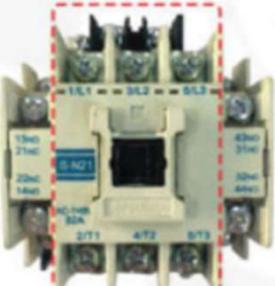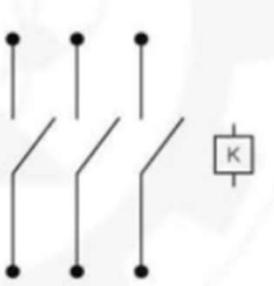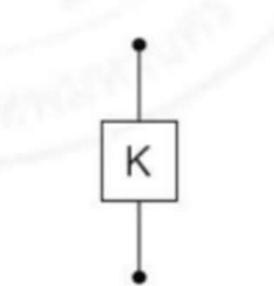ลักษณะ	วงจรไฟฟ้า
	 <p>NC NO</p>
	 <p>K</p>
	 <p>K</p>

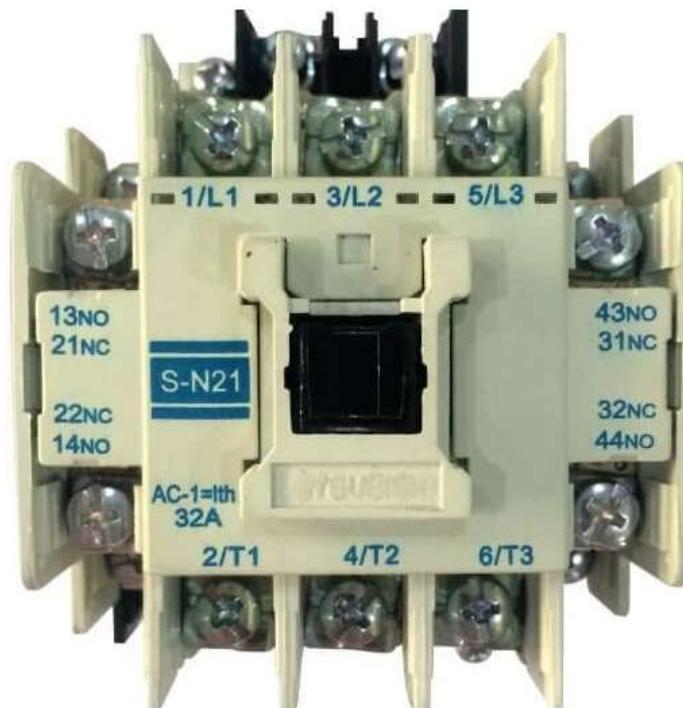

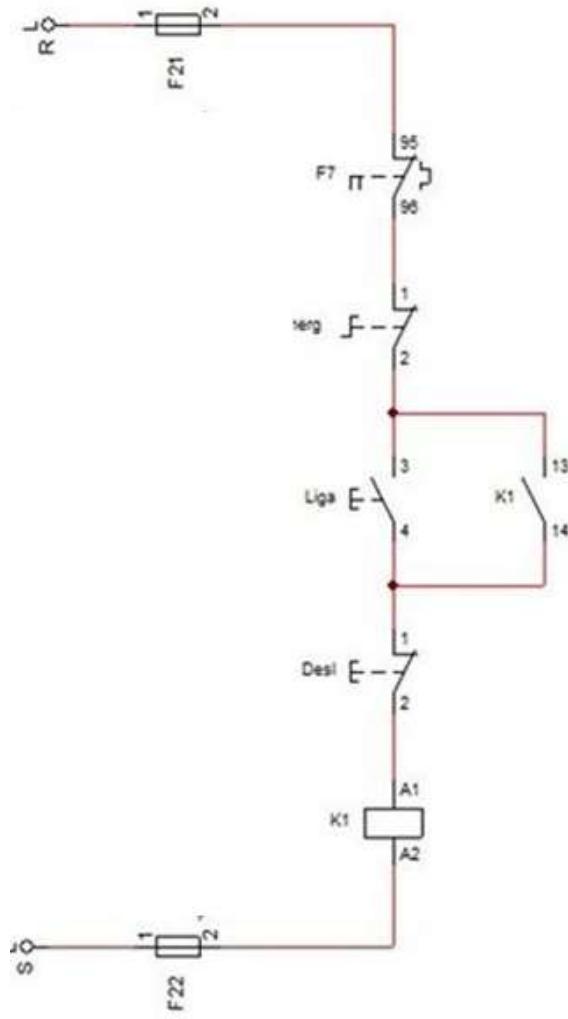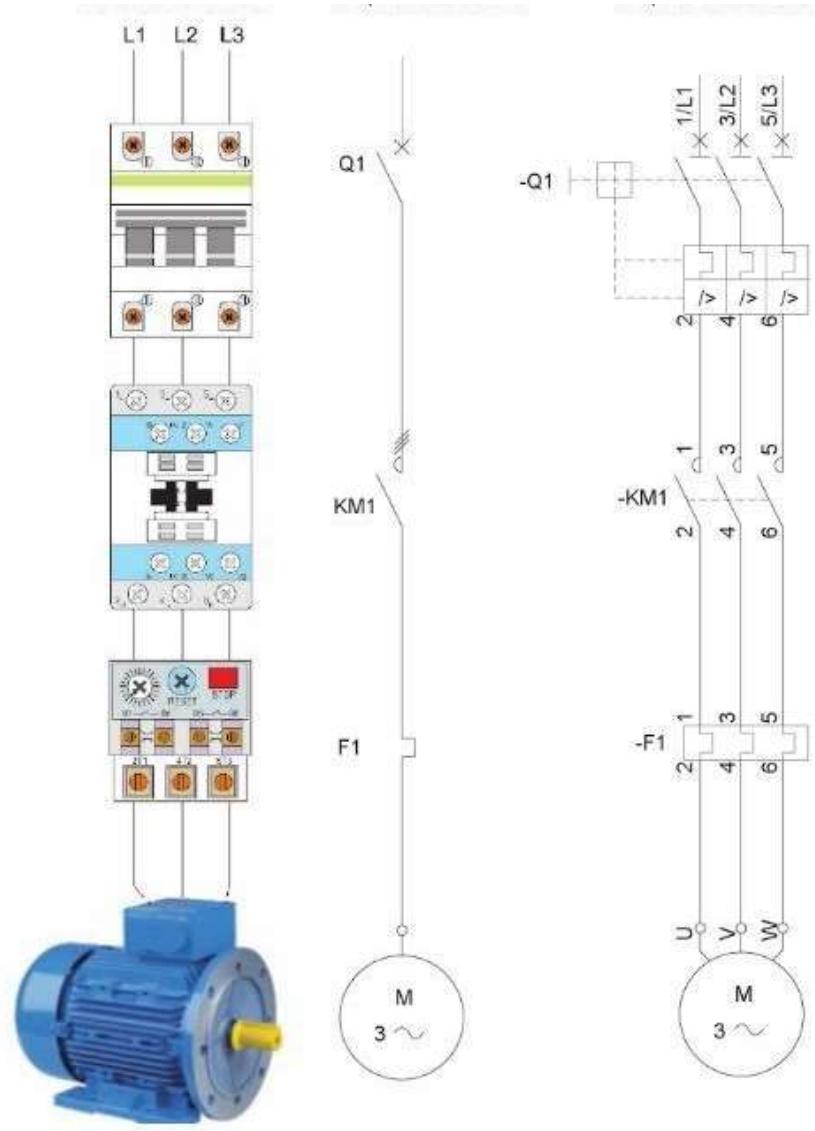



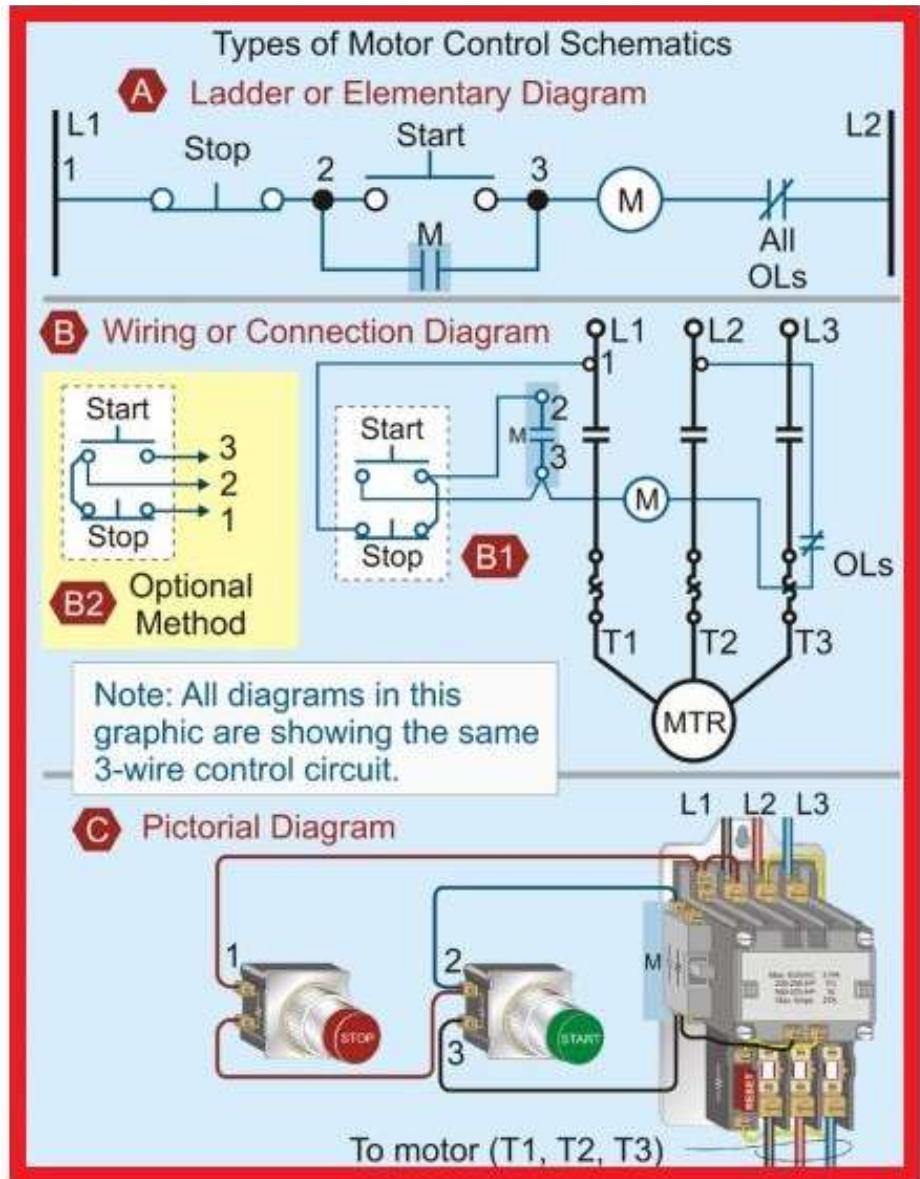
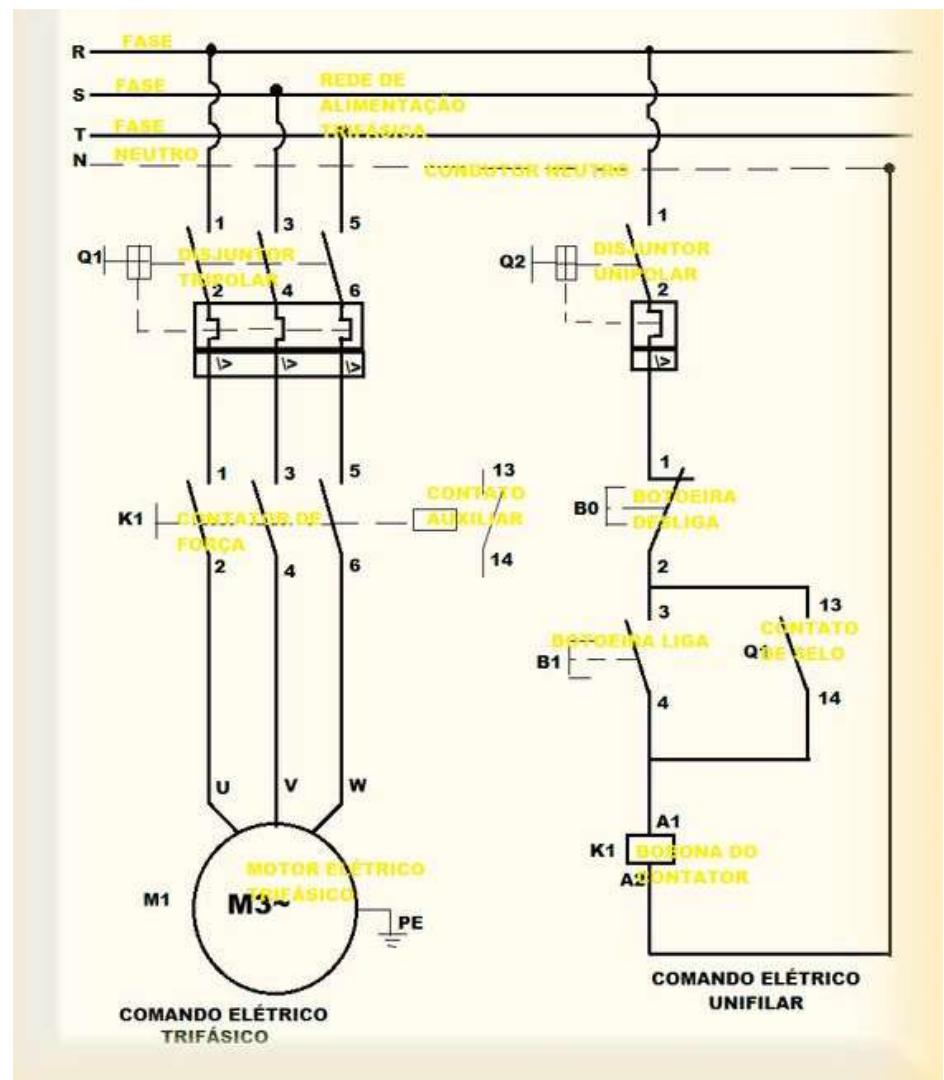


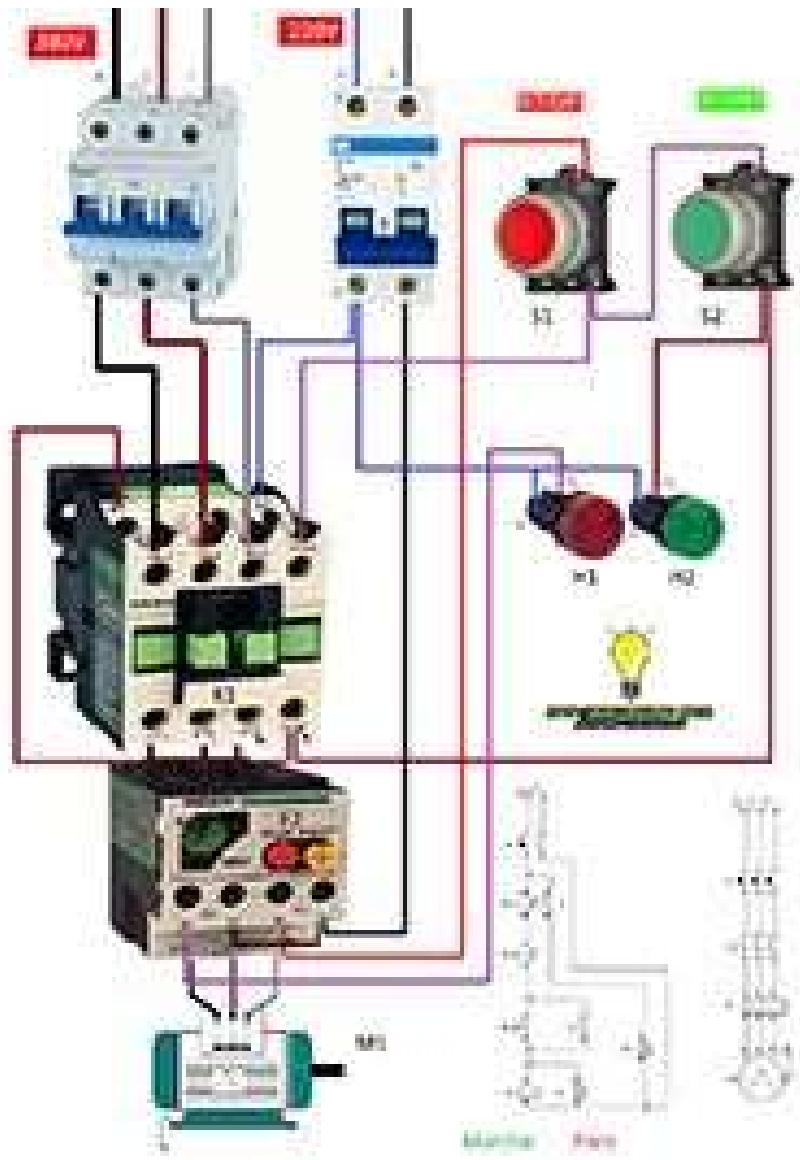

Red eléctrica trifásica

3N+PE ~ 400V


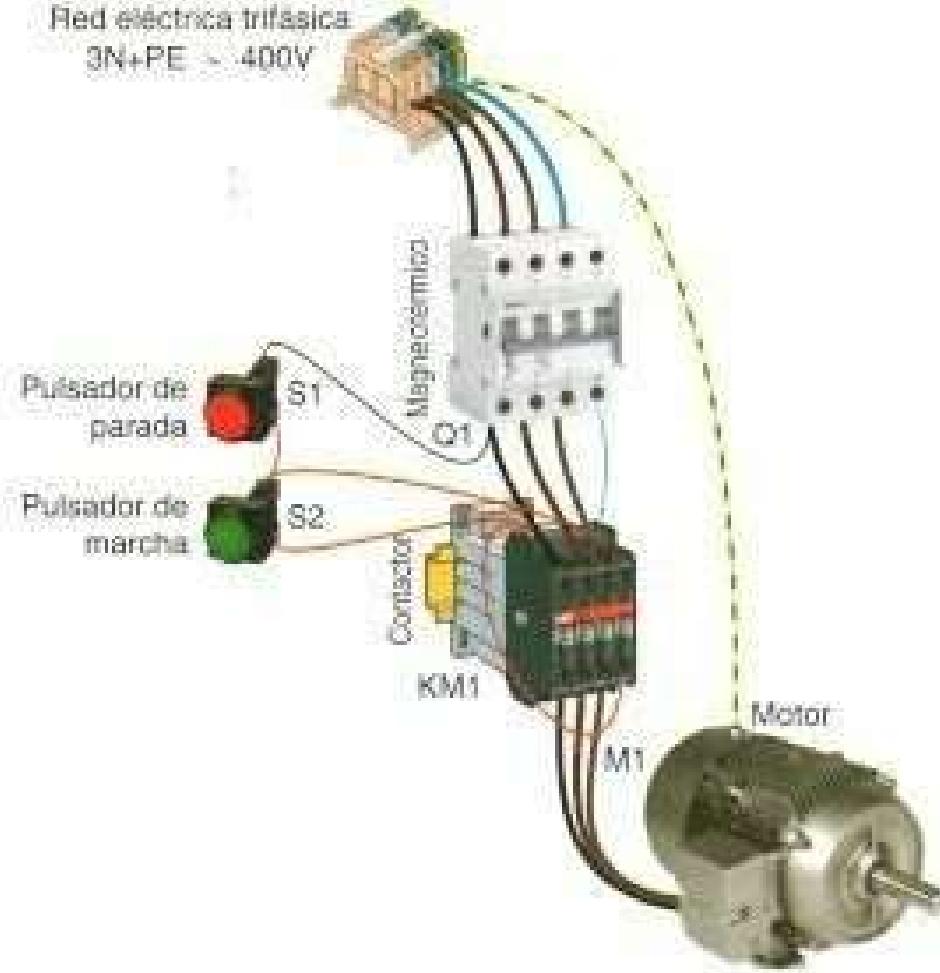


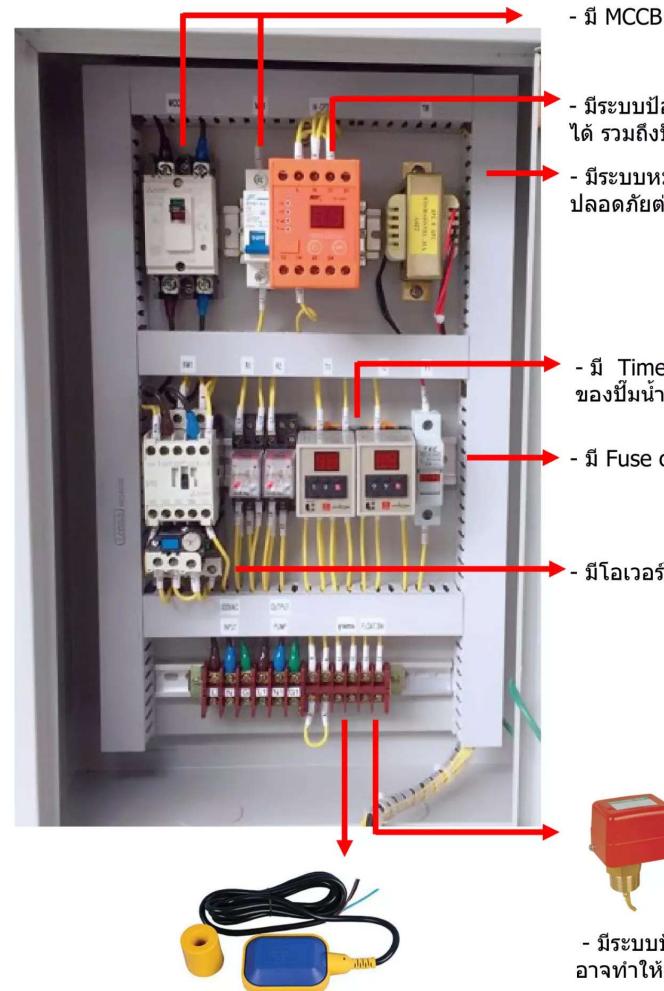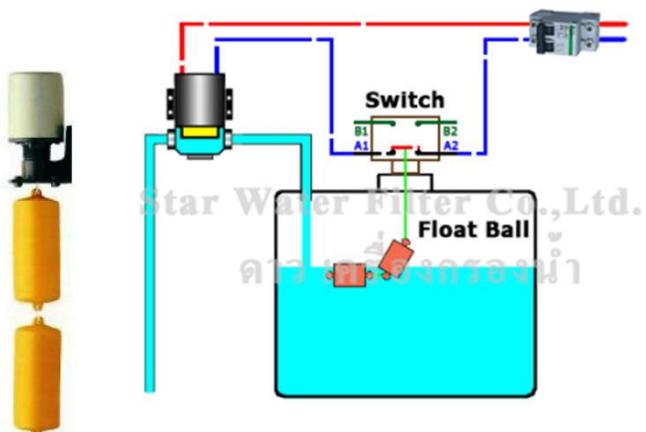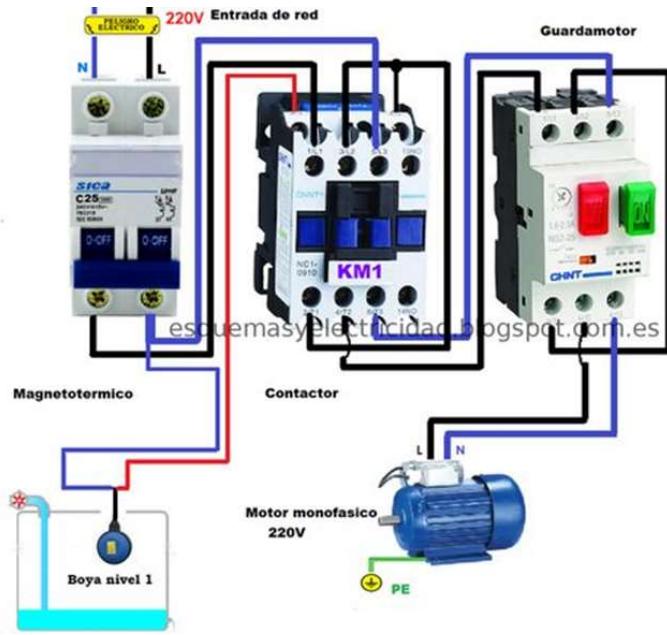


- มี MCCB , MCB ป้องกันการลัดวงจร
- มีระบบป้องกันไฟตกไฟเกิน เพื่อไม่ให้อุปกรณ์ภายในตู้เสียหายได้ รวมถึงปั๊มน้ำด้วย
- มีระบบหน้อแปลงไฟจาก 220vac เป็น 24vac เพื่อความปลอดภัยต่อผู้ใช้งาน
- มี Timer หน่วงเวลาซึ่ครรบบัน้ำในเส้นท่อ แล้วกลับมาทำงานของปั๊มน้ำแบบอัตโนมัติ
- มี Fuse control ป้องกันการลัดวงจรแรงดันต่ำ
- มีโอเวอร์โหลดดิจิตอล ป้องกัน การกินเกินกระแสอเดอร์
- มีระบบป้องกันปั๊มน้ำ Run dry เพื่อไม่ให้ปั๊มน้ำทำงานตัวเปล่า อาจทำให้ปั๊มน้ำเสียหายได้ ด้วย ไฟสวิทช์


Float Switch

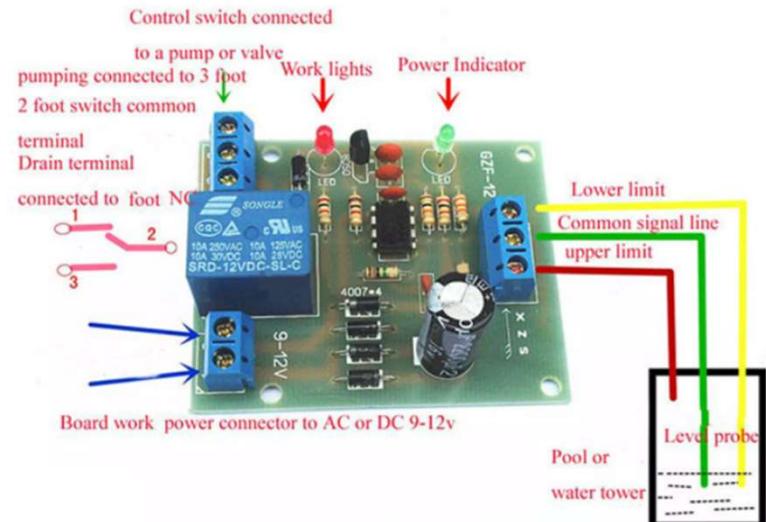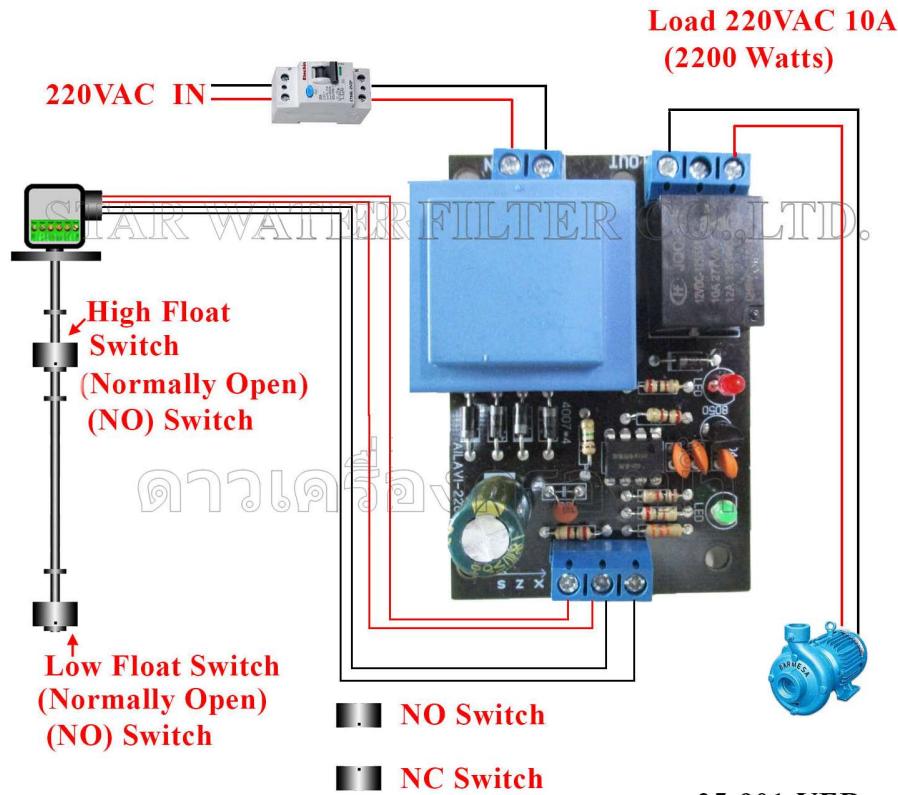High Low Water Level Controller Module 10A 220VAC






Physical Diagram Installation

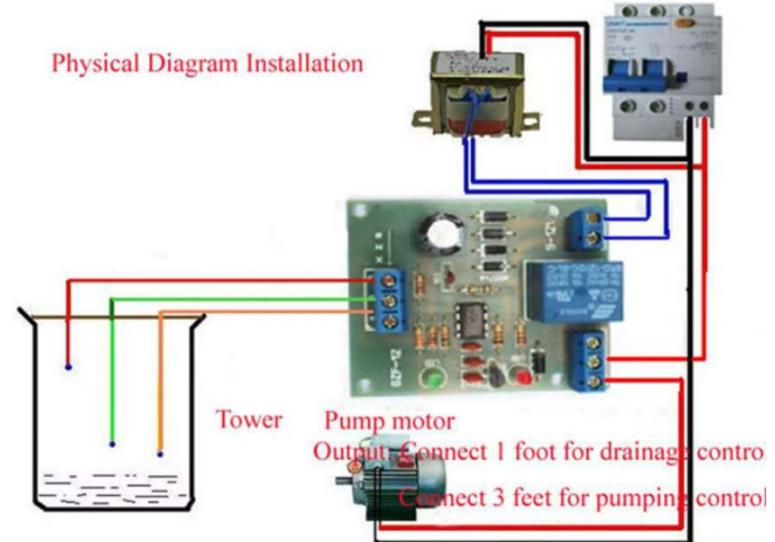

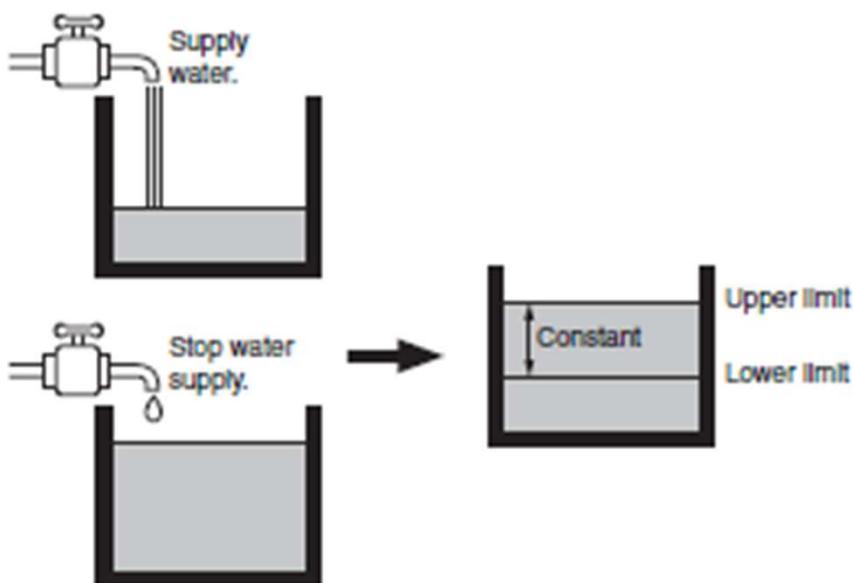


Theory	61F Controller
<p>No current flows.</p>	<p>0V 24V U</p> <p>200V</p> <p>61F-11N Relay Unit</p> <p>Relay Contacts</p> <p>Electrodes</p> <p>E3</p> <p>E1</p> <p>No current flows.</p>

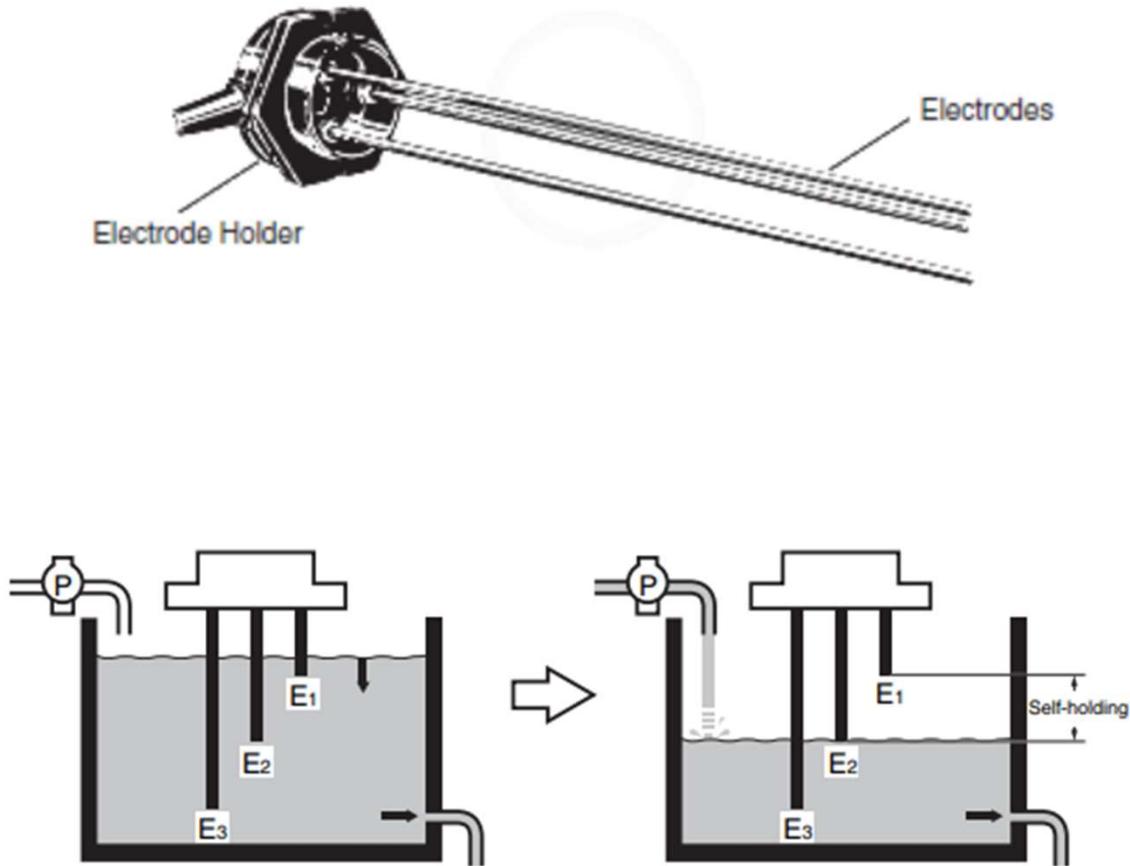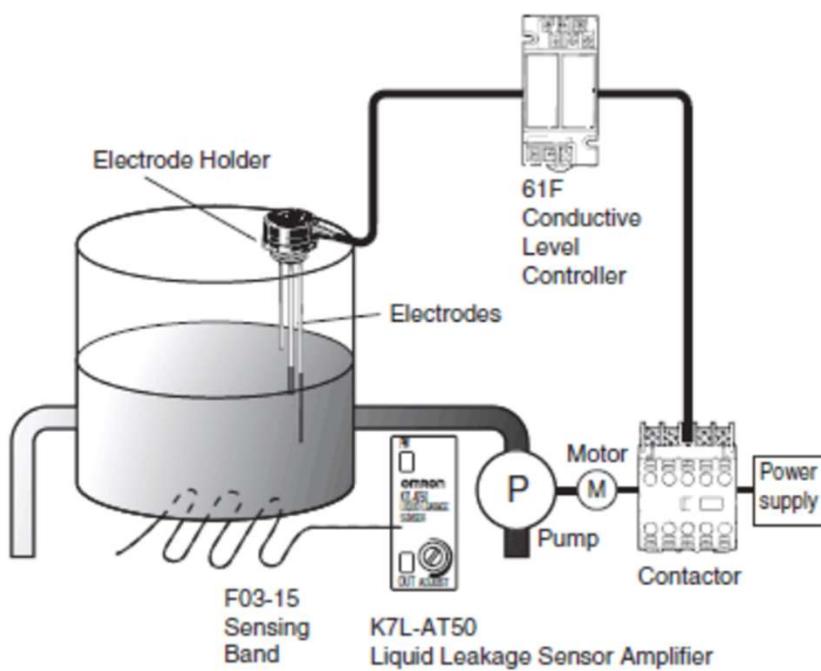

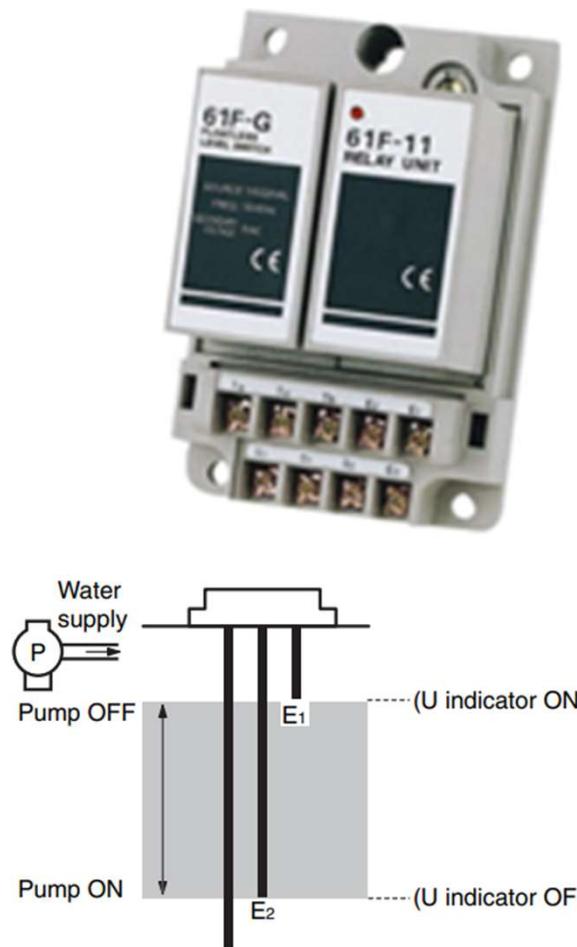

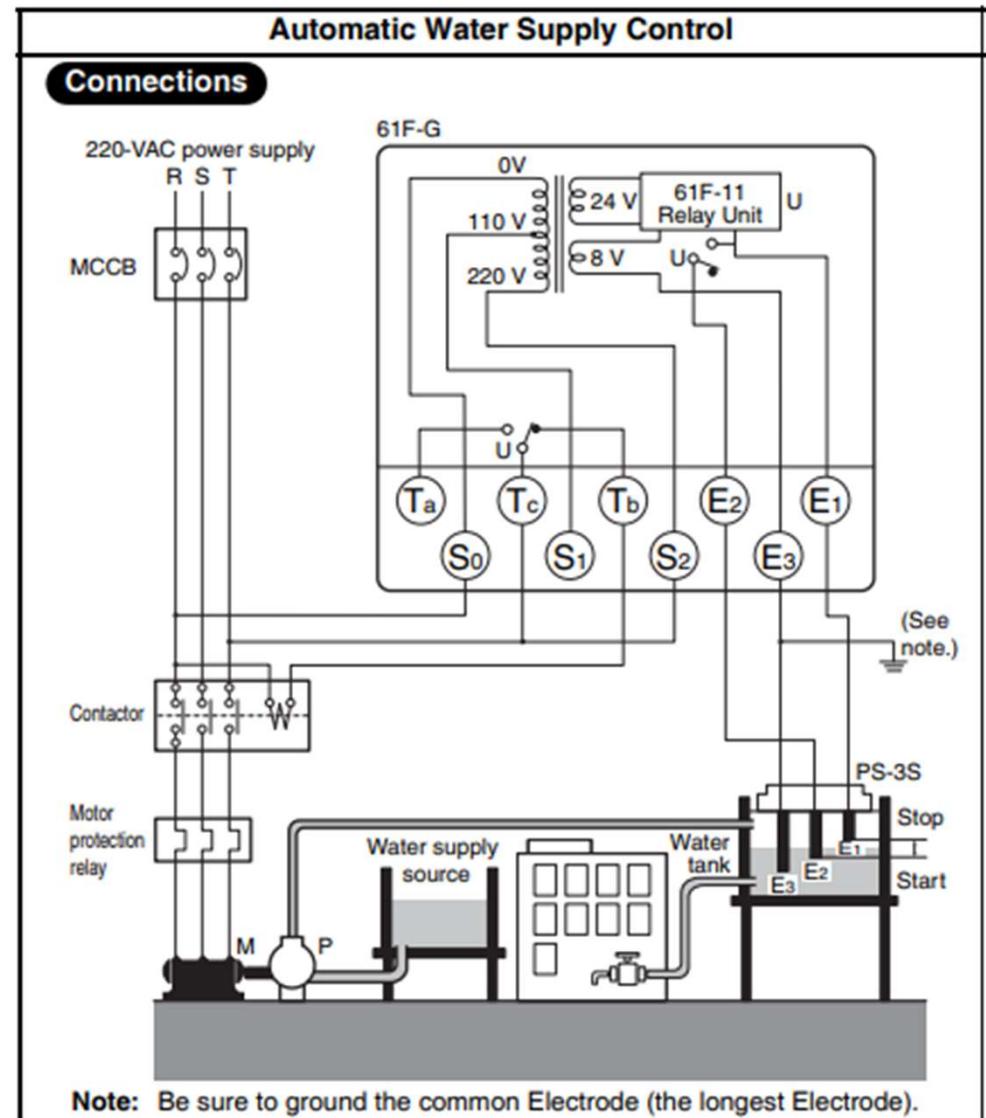
- Connect Tb to the contactor's coil terminal.
- Power Supply Connections (for models with 110/220-V power)
 - 110 VAC: Connect S₀ and S₁.
 - 220 VAC: Connect S₀ and S₂.



Basic Type

61F-G1

Dimensions:
page 14

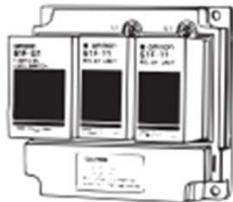

CAUTION (ご注意)
1. 110V: S₀-S₁
220V: S₀-S₂
2. No testing dielectric strength.
across each electrode terminal.
(電極端子間での耐電圧テスト禁止)

Automatic Water Supply Control with Pump Idling Prevention

Connections

220 VAC power supply

R S T
MCCB

0 V
110 V
220 V

24 V
24 V
8 V

U₁
U₂
U₁'
U₂'

S₀
S₁
S₂
E₃
E₂
E₁
E₂'
E₁'
(E₄)

T_{b1}
T_{a1}
T_{c2}
T_{b2}
T_{a2}

B
Alarm

Contactor

(See note.)

Motor
protection
relay

M

P

E₃'
E₂'

PS-3S
Water
supply
source

E₁'
E₂'

PS-3S
Water
tank

E₁
E₂

Stop

Start

Push
button
switch



PS-3S

Water
tank




E₃
E₂

Start

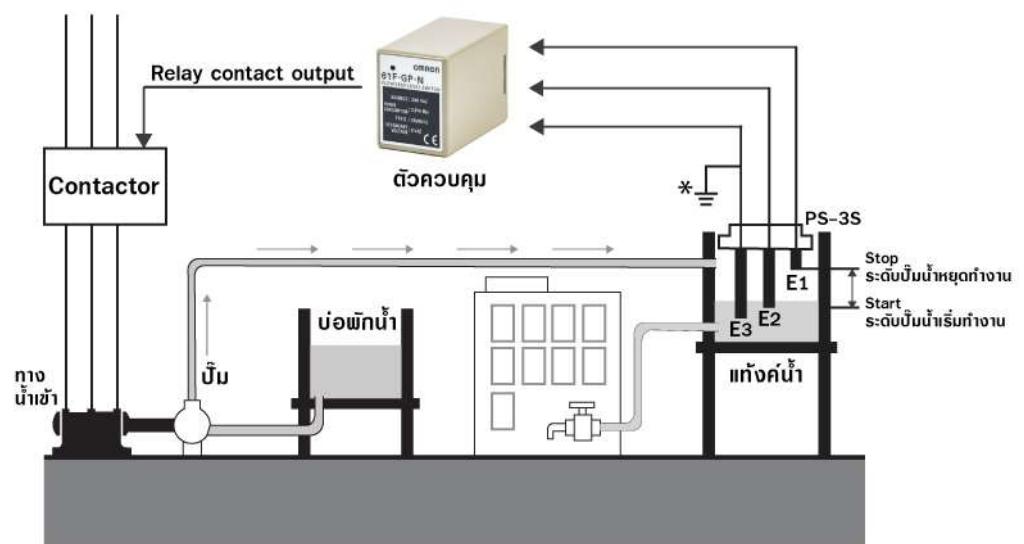
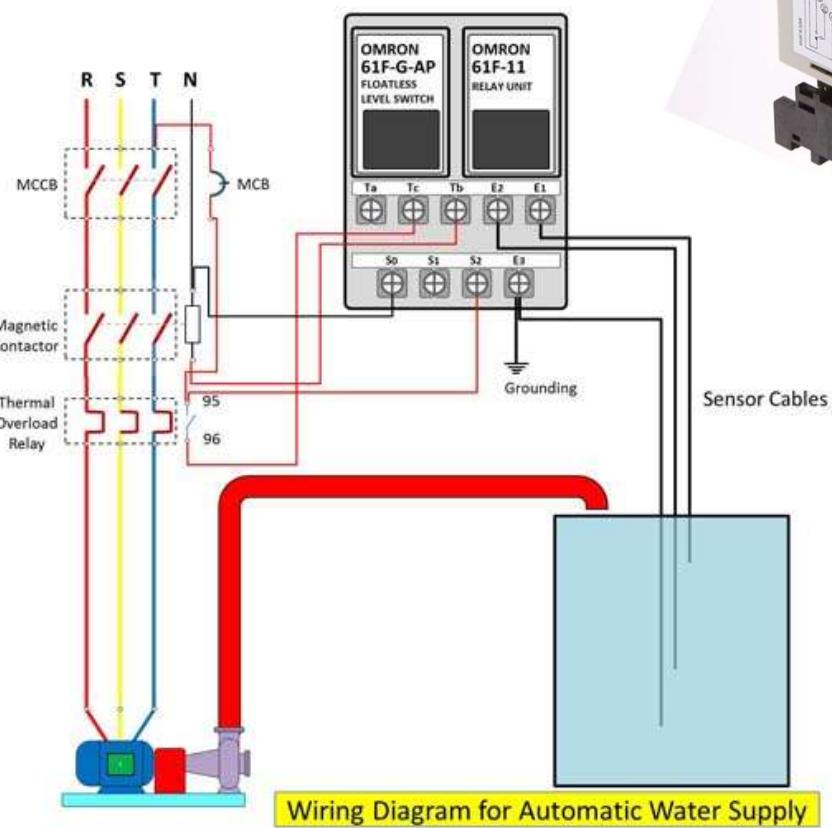
Note: Be sure to ground the common Electrode (the longest Electrode).






Solenoid Valves

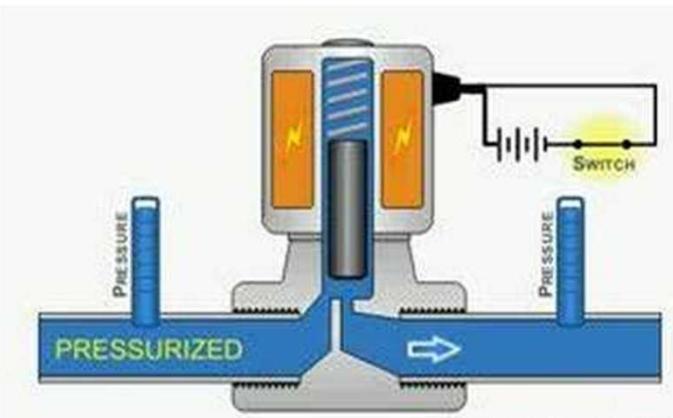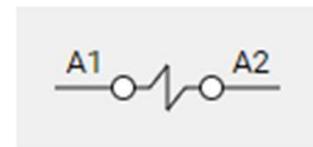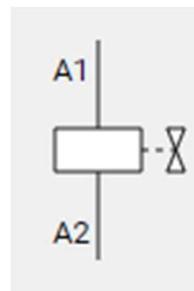



ระบบประดับน้ำอัตโนมัติ 4 โซน

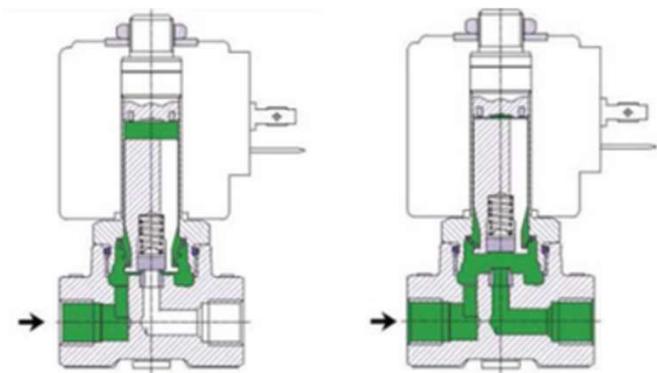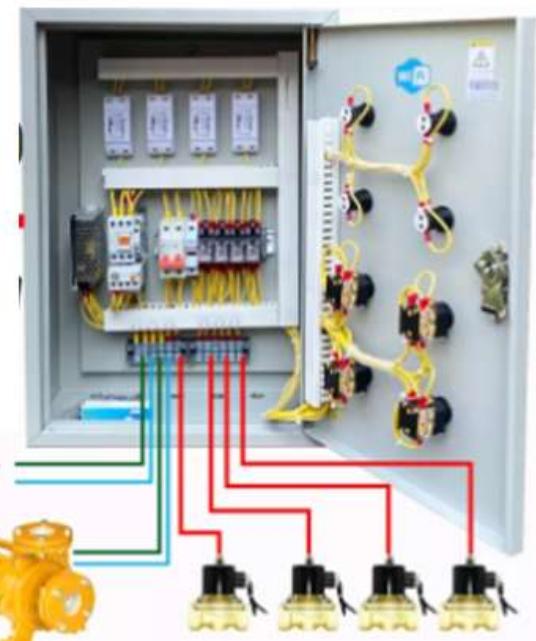




Solenoid Valves

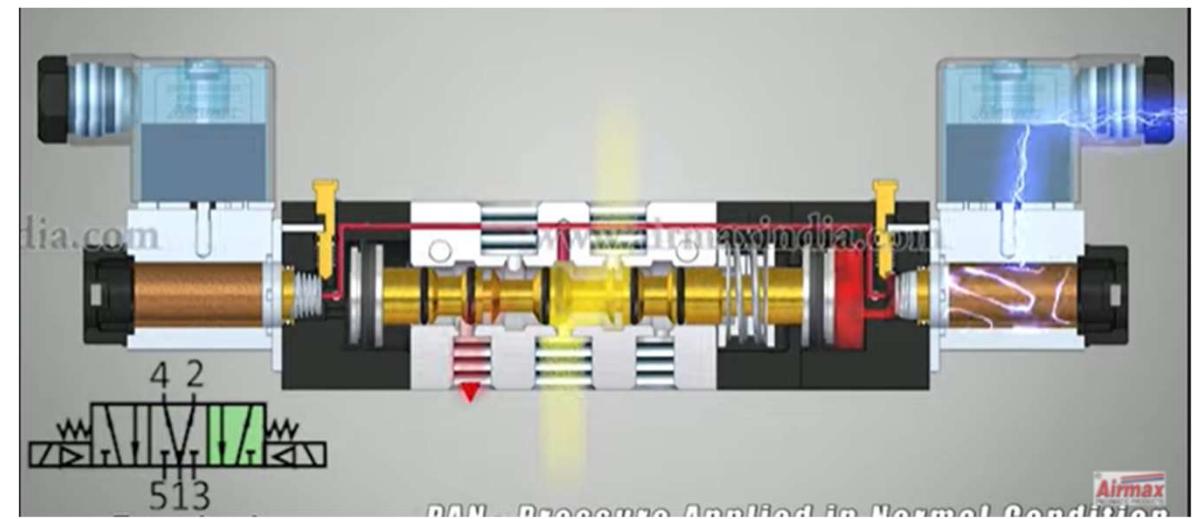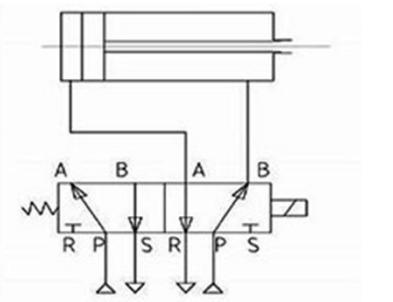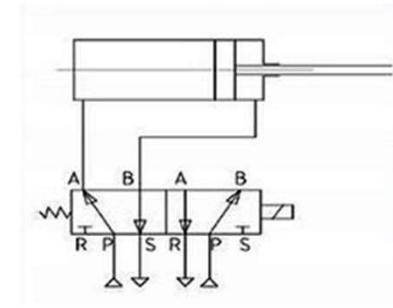


IOT

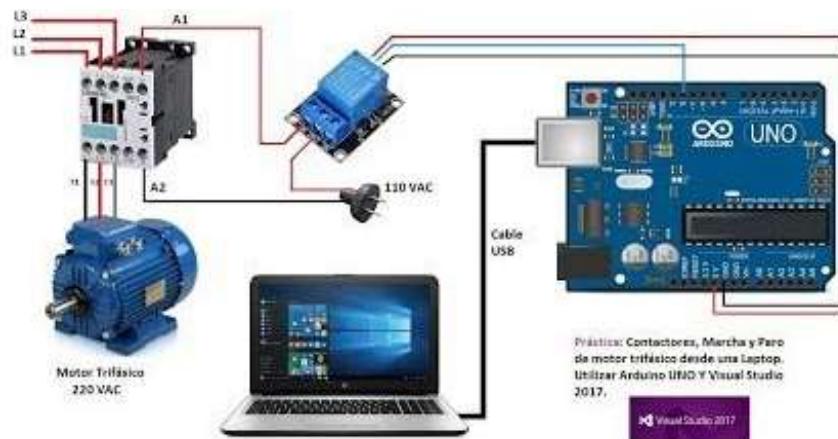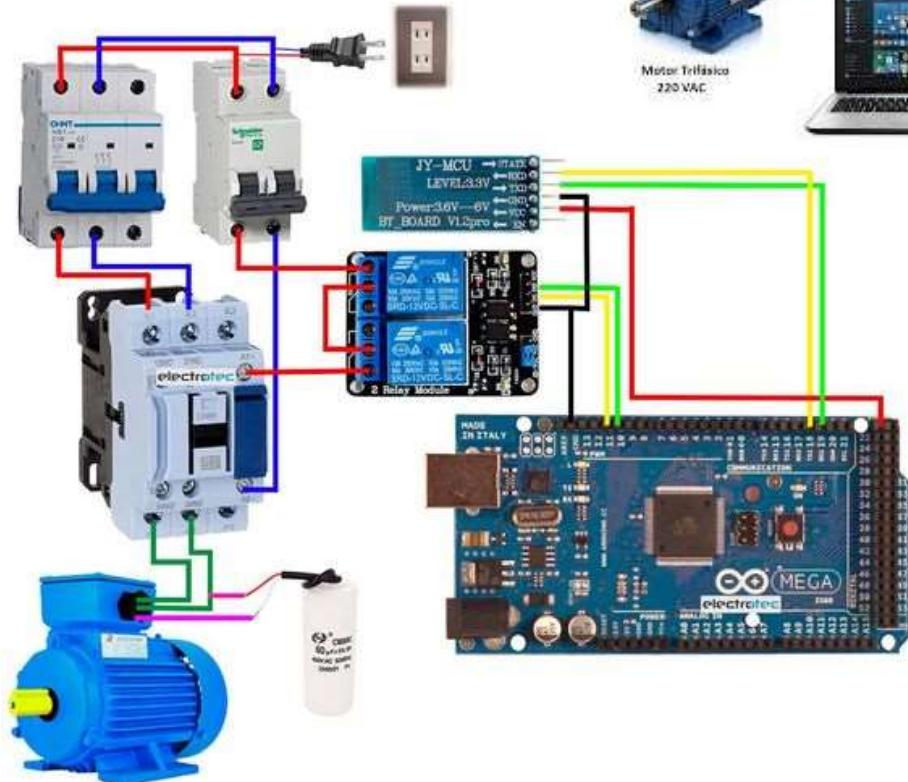

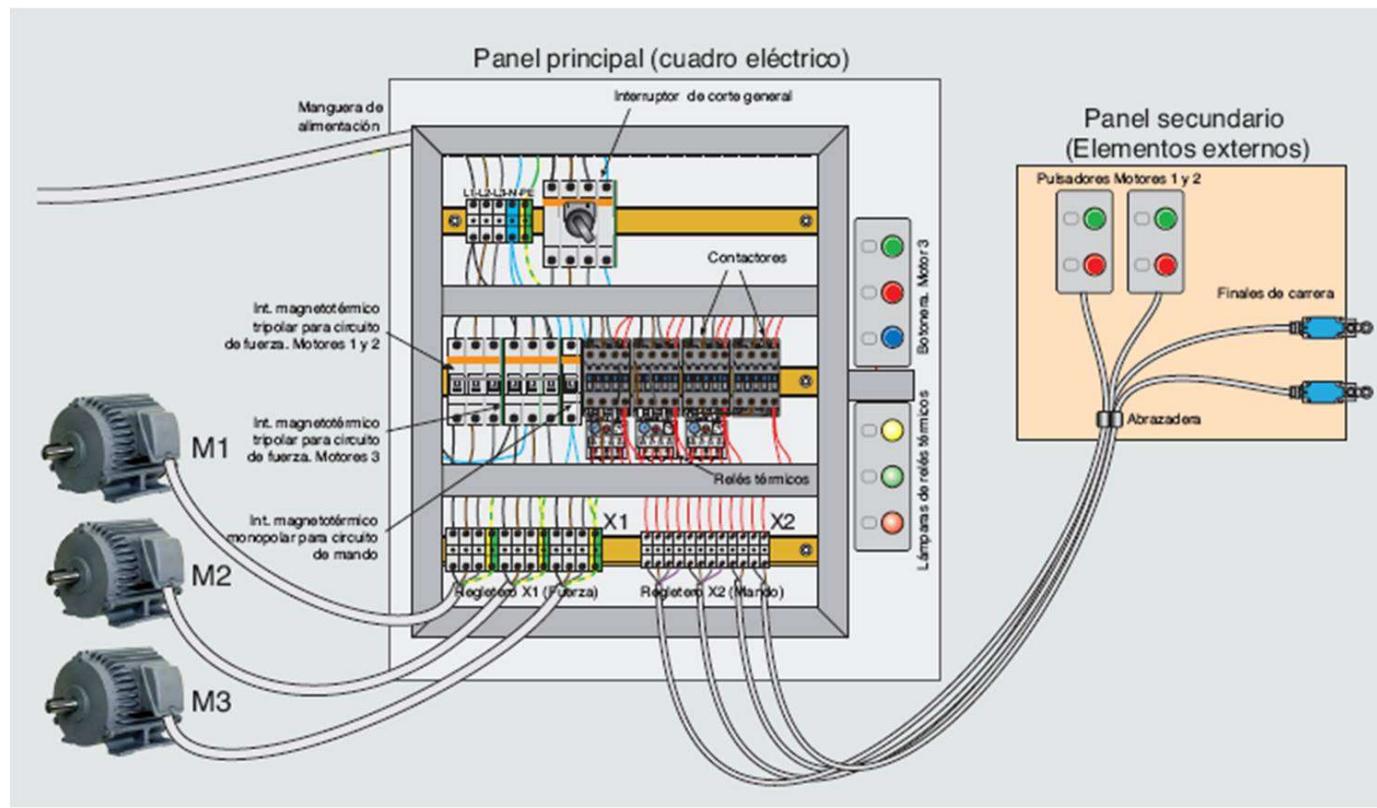


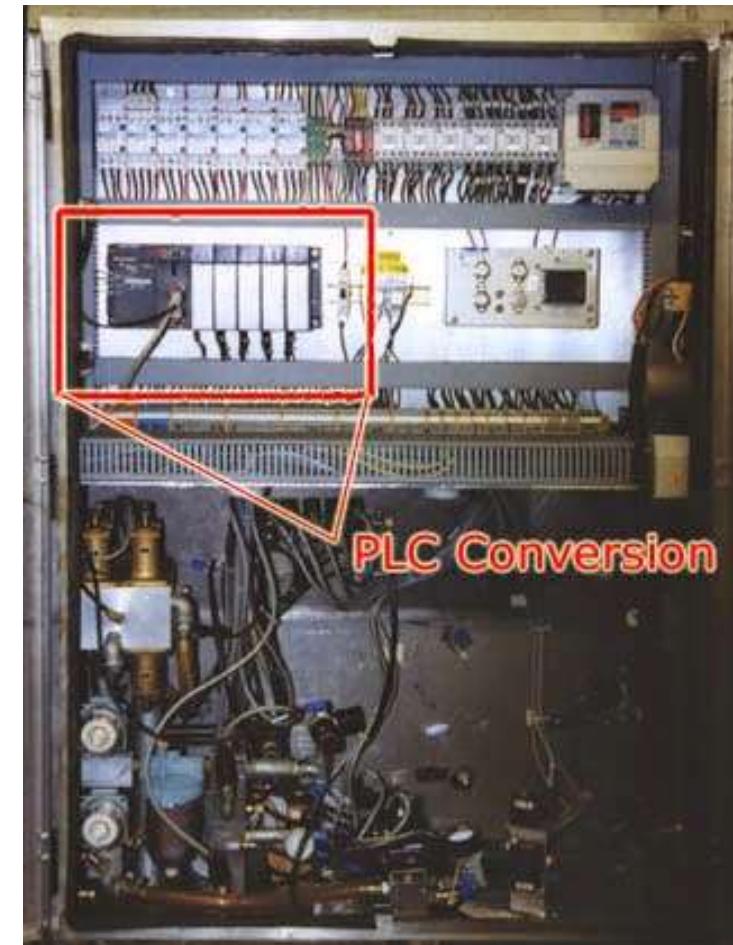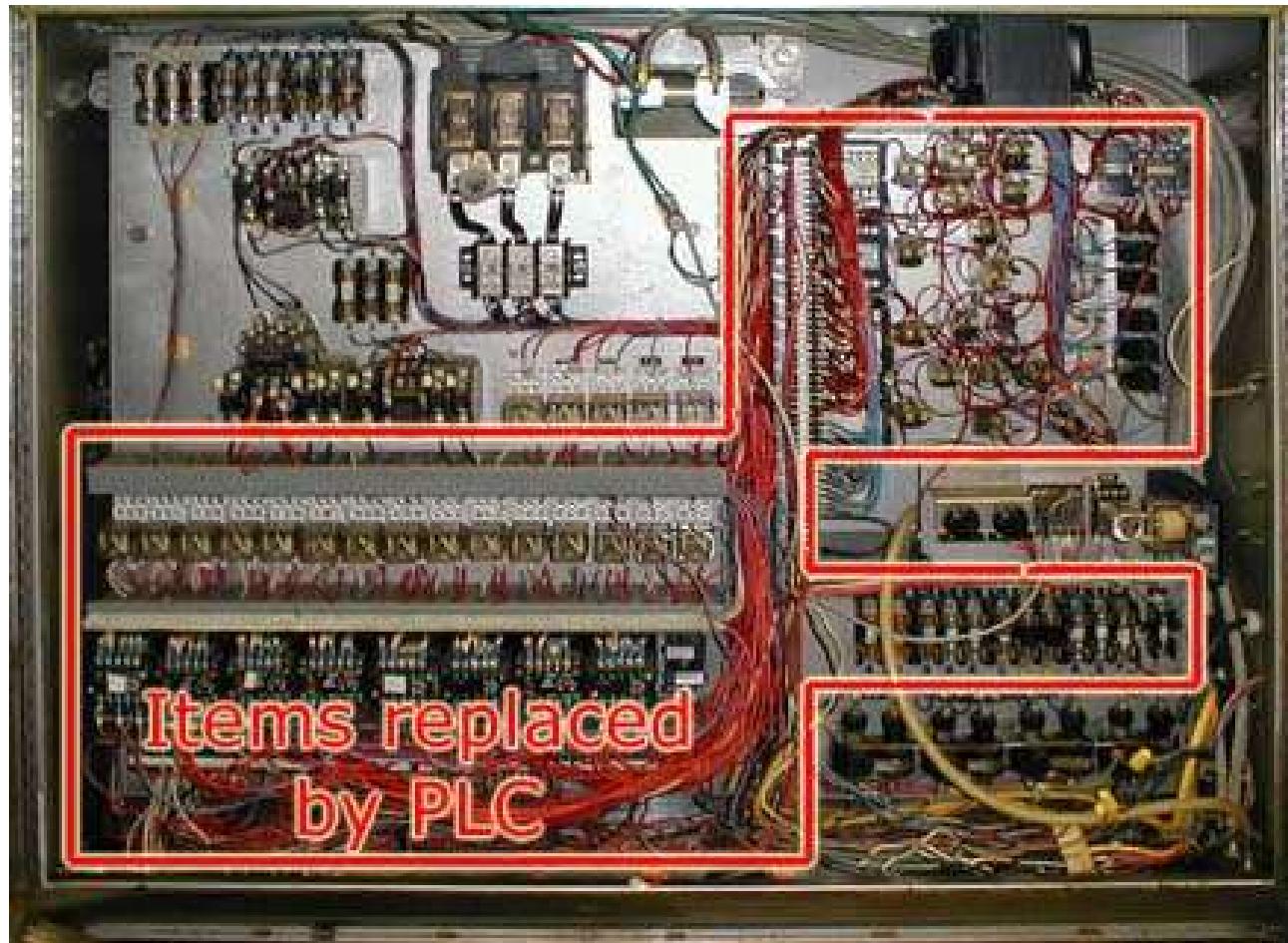


PLC (Programmable Logic Control)

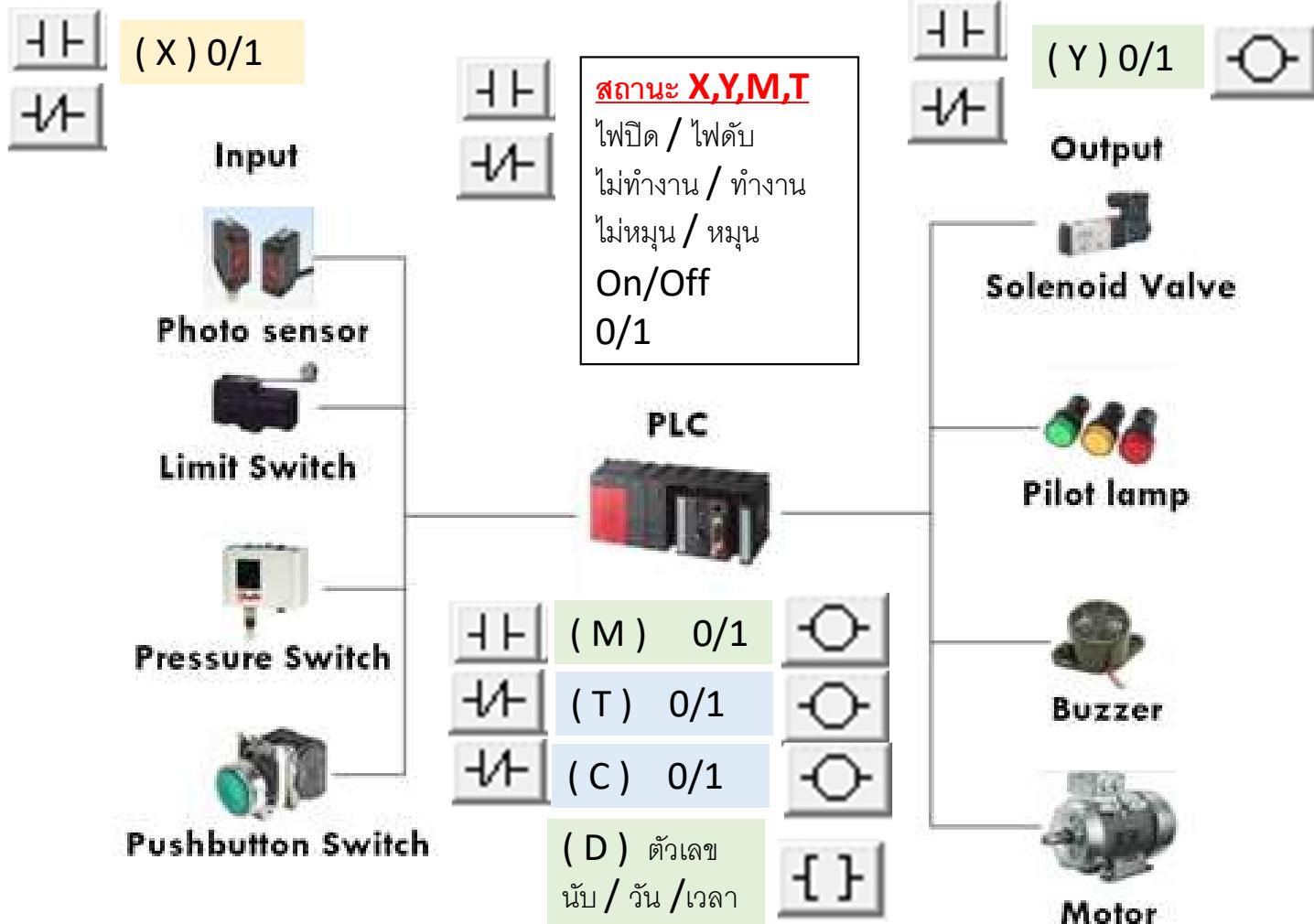

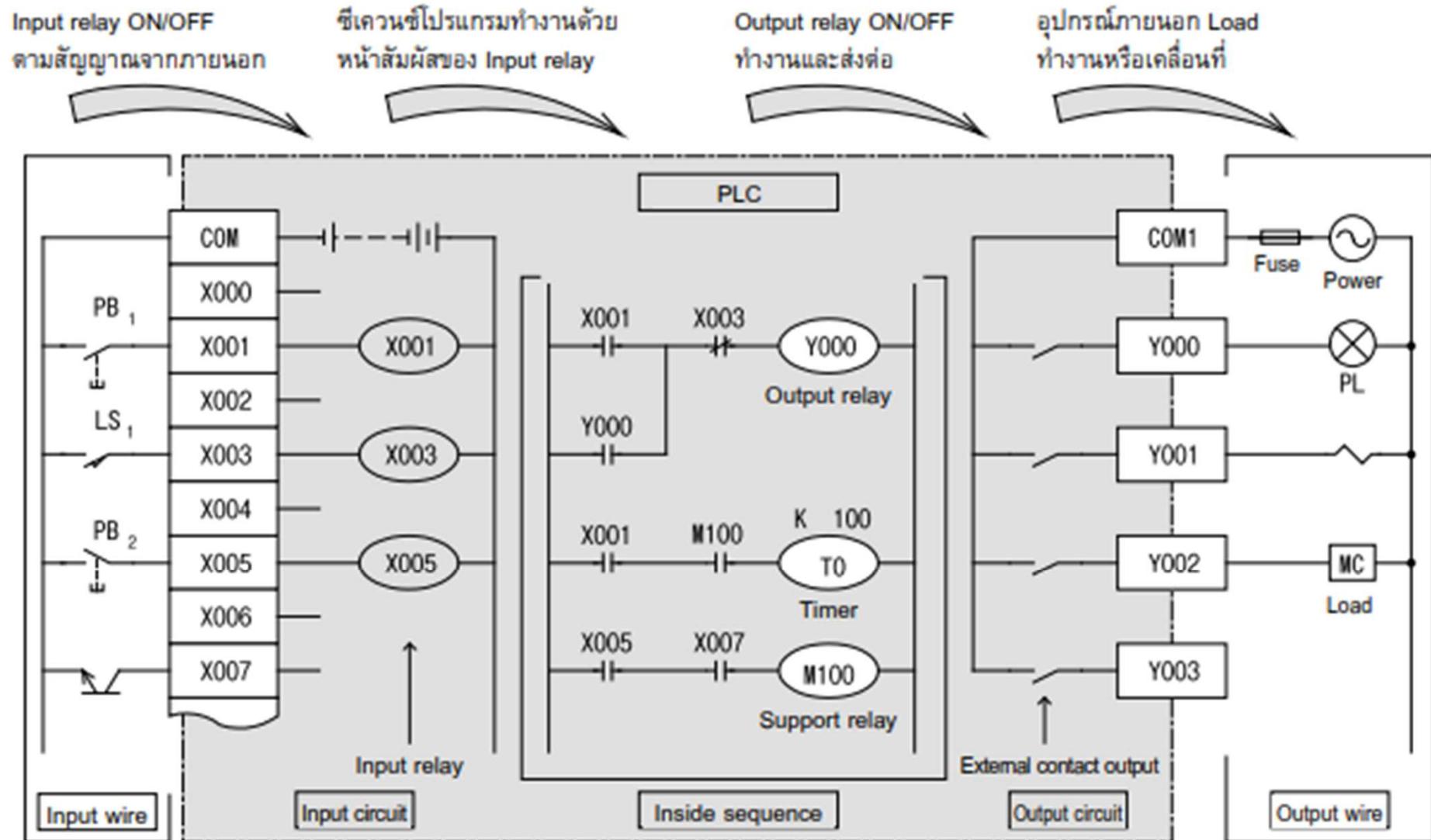- (X) Input
- (Y) Output
- (M) Mem Relay
- (T) Timer
- (C) Counter
- (D) Memory



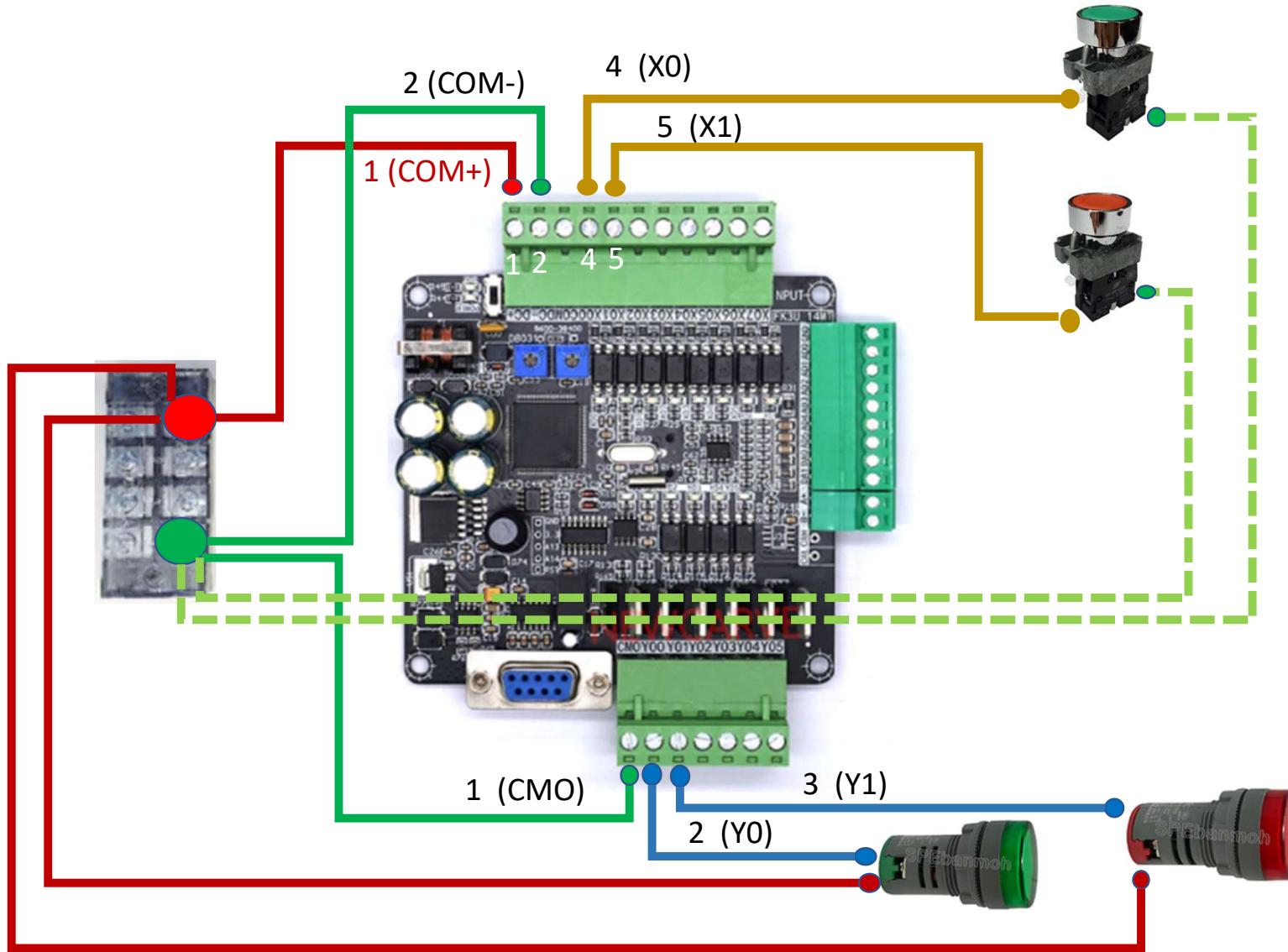

FXTRN

SW0D5C-FXTRN-BEG-E

File Edit Simulation Tools Help

[A] Let's Learn the FX Series PLC [B] Let's Study the Basics [C] Easy Does It! [D] Beginner Challenge [E] Intermediate Challenge [F] A ◀ ▶

B-1. Basic I/O Program

Learn input and output programs.

1 star

B-2. Standard Program

Learn a latched output program and SET/RST program.

1 star

B-3. Control Precedence Program

Learn an interlock program which controls conflicting operations.

1 star

B-4. Reading the Input Status

Learn how to initiate instructions at the detection of rising or falling edge of a pulse.

2 stars

PLC 01 – NO NC Contact youtube

SW0D5C-FXTRN-BEG-E


File Edit Simulation Tools Help

Basic I/O Program

The screenshot shows a PLC programming interface with the following components:

- Ladder Logic Area:** Displays two parallel rungs. Rung 1: Input X020 (NO contact) connected to output Y000. Rung 2: Input X021 (NC contact) connected to output Y001.
- Output Area:** Shows three outputs: Y0 (Operating), Y1 (Stop), and Y2 (Error).
- Operation Panel:** A window titled "Operation Panel" containing:
 - Lamp display:** Four indicator lights labeled PL1, PL2, PL3, and PL4, each corresponding to an output (Y20, Y21, Y22, Y23).
 - Operation switches:** A group of buttons and switches including PB1-PB4, X20-X25, SW1-SW2, and two analog potentiometers labeled X23 and X24.
- Bottom Navigation:** Includes tabs for Project, Edit, Convert, View, Online, Tools; a RUN button; and a status bar with memory addresses like Com cF5, F5, F6, sF5, sF6, F7, F8, F9, sF9, oF9, cF10, sF7, sF8, aF7, aF8, caF10, F10, aF9.
- Status Bar:** "Write data to the PLC" and "RUN".

PLC 02 – Self Holding youtube

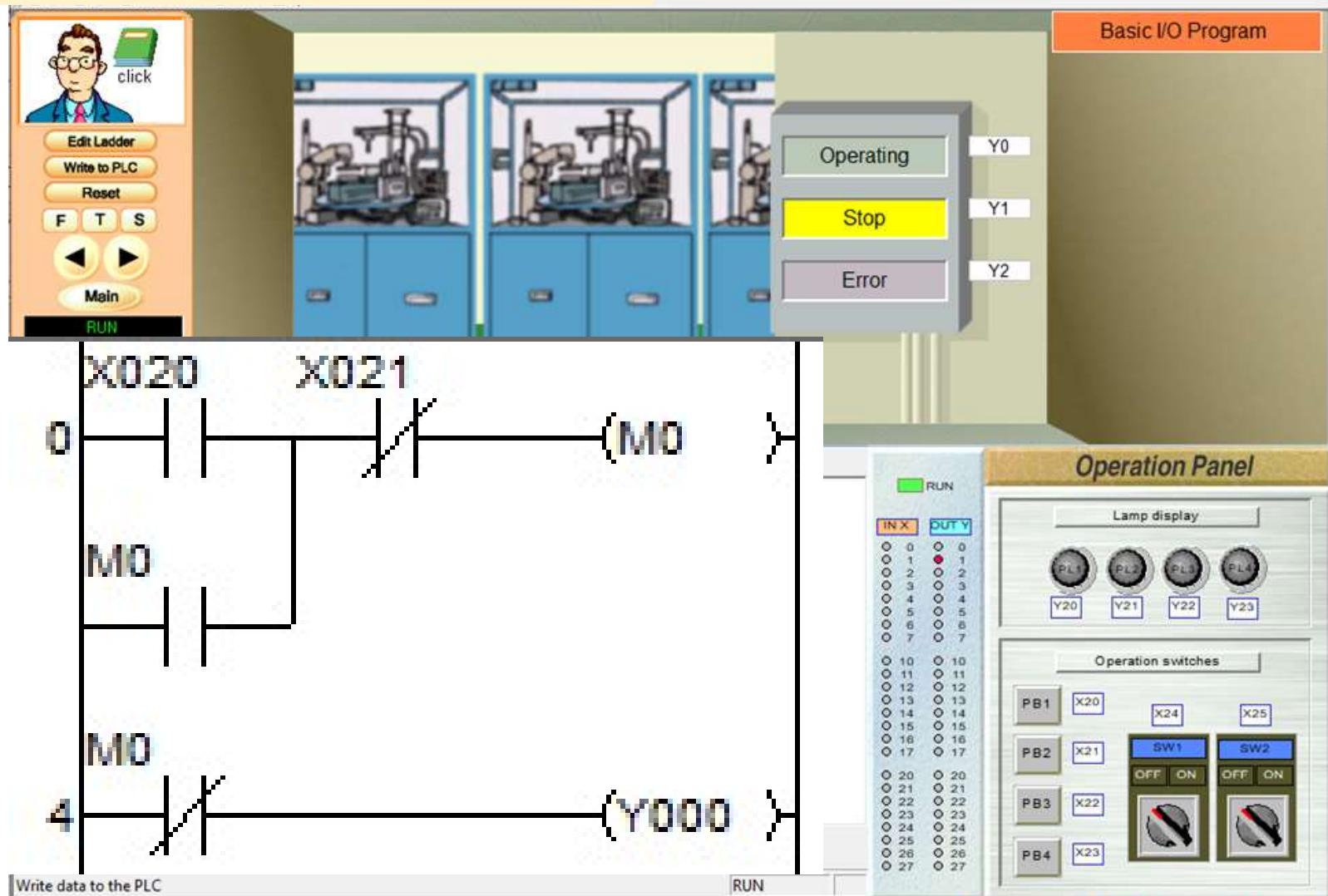

C-1. Basic Timer Operation

Learn the On-delay time function.



C-3. Application Timer Program - 2

Learn a "flicker" program
executed by timers.



C-2. Application Timer Program -1

Learn the Off-delay time function
and the one shot timer.



C-4. Basic Counter Program

Learn control methods using counters.



PLC 03 – Basic Timer youtube

File Edit Simulation Tools Help

Basic Timer Operation

X0(Lower limit) Y0(Door up command)
X1(Upper limit) Y1(Door down command)

Y5(Red)
Y6(Green)
Y7(Yellow)

Timer

3 Press the [F4] key to convert the program you have input.

Ladder logic:


```
LD
    X020      ( T0 ) K30
    T0        ( Y000 )
    X021      ( T1 ) K40
    T1        ( Y001 )
```

Control buttons:

- PB1 X20
- PB2 X21

Enter symbol

- () - T0 K30

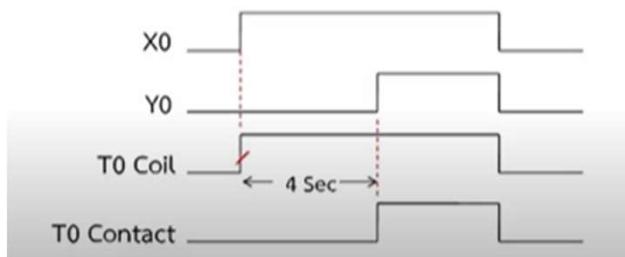

PLC 04 – Open and Close Door YouTube

SW0D5C-FXTRN-BEG-E

File Edit Simulation Tools Help

click

Edit Ladder
Write to PLC
Reset
F T S
Main
RUN

```
graph TD; X020[0] ---|X020| X001[X001]; X001 ---|X001| Y000["Y000 >"]; X021[4] ---|X021| X000[X000]; X000 ---|X000| Y001["Y001 >"];
```

X1(Upper limit)

Y5(Red)
Y6(Green)
Y7(Yellow)

Y0(Door up command)

Y1(Door down command)

X0(Lower limit)

PB1 X20

PB2 X21

Basic Timer Operation